

Dated : \_\_\_\_\_

(Week-1)

## Atomic Structure.

### Atom

Atom is the basic particle of an element, and all matters.

- Each element has different atomic structure.
- Atom consists of proton, neutron, & electron.

- Atom has shells & shell

consists of orbits

- Shell = K, L, M, N.

$$\text{Orbits} = K_s (s) = 2 \text{ elec} = 2$$

$$L_s (s,p)_{\text{orb}} = 2, 6 = 8$$

$$M_s (s,p,d) = 2, 6, 10 = 18$$

$$N_s (s,p,d,f) = 2, 6, 10, 14 = 32$$

- Orbit shows different energy levels.

- Outermost shell Valence shell, electrons

Valence electron, escaped electrons free electrons.

## Matter Classification.

- 1- Conductors.
- 2- Insulators.
- 3- Semi-Conductors.

### Conductor.

- Conductor is a material that allow easily flow of electrical current,
- best conductors — single element materials



copper, silver, gold, aluminum.

Electron in valence shell, easily breakable.

$$\begin{aligned}\text{Proton} &= 2 \text{ up quarks} \\ \text{charge} &= 1 \text{ down} \\ \frac{2}{3} + \frac{2}{3} - \frac{1}{3} &= 1\end{aligned}$$

$$\begin{aligned}\text{Neutron} &= 2 \text{ down} - \frac{1}{2} \\ &= -\frac{1}{3} - \frac{1}{3} + \frac{2}{3} \\ &= 0\end{aligned}$$
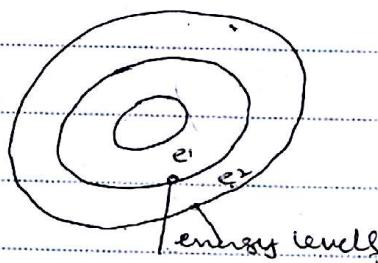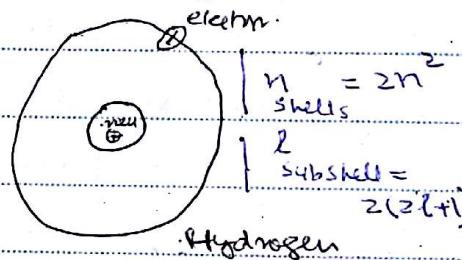
$$\begin{aligned}\text{Electron} &= 3 \text{ down} (-\frac{1}{3}) \\ &= -\frac{1}{3} - \frac{1}{3} - \frac{1}{3} = -1\end{aligned}$$



## Insulators.

do not



- Insulators are material that ~~cannot allow~~ allows flow of current under normal conditions.
  - good insulators are compound material, wood, glass, diamond.
  - Valence electrons tightly bond.

## ² Semi-Conductors.

- Semi-conductors are materials which conduct b/w Conductors & insulators.
  - pure semi-conductors are not good conductor nor good insulators. Carbon<sub>6</sub>, silicon<sub>14</sub>, Germanium<sub>32</sub>. Valence electron = 4.
  - Pure semi-conductors = Intrinsic semi-conductors
  - Impure semi-conductors = Extrinsic semi-conductors.
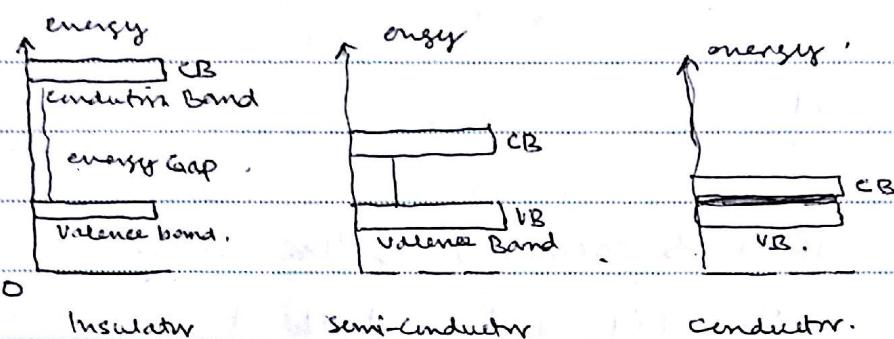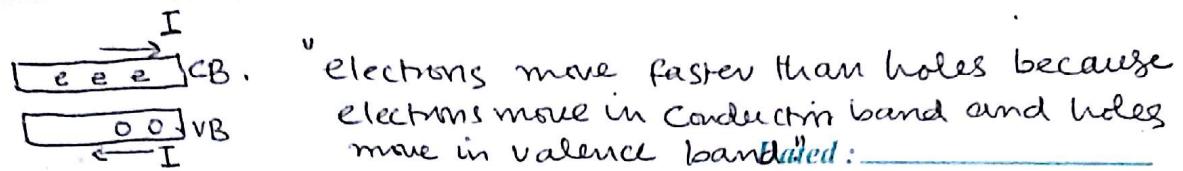
## Energy-Band,

- Energy-band basically shows energy levels of the electron.
  - Bond formed by energy levels of valence electron is called Valence Band.
  - When atom is excited and valence electron escape, becomes free electron, the region is known as Conduction Band.
  - Region b/w VB & CB is forbidden Band.



- For insulator difference / distance between VB & CB is large and electron cross if breakdown condition reaches  $\rightarrow$  Large (extreme) Voltage.


- For Semi-conductor

Germenium = 0.7ev ( energy require )

Silicon = 1.1ev

O Super-conductor.

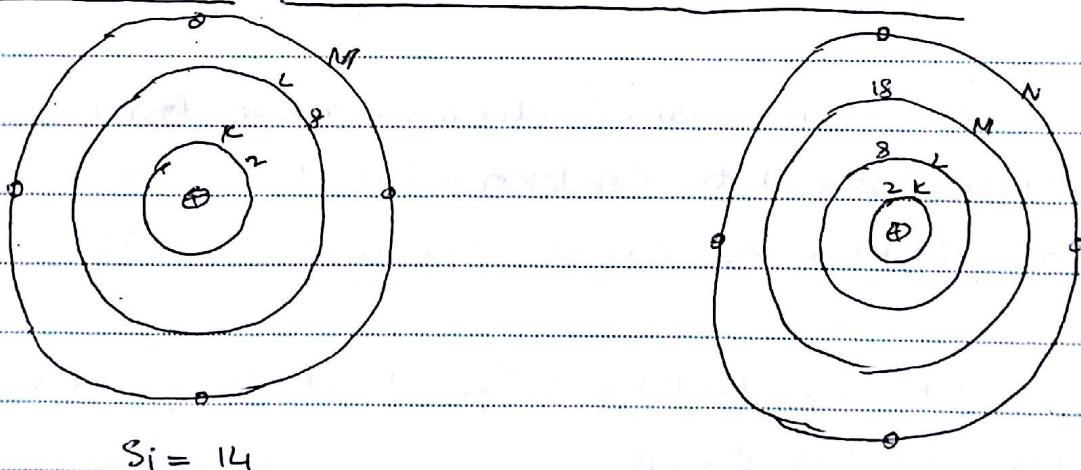
### Atomic Structure of Silicon & Germanium.



- Valence electrons in Germanium = 4<sup>th</sup> shell.
- Valence electrons in Silicon = 3<sup>rd</sup> shell.
- So Germanium electrons are at higher energy levels that why require less energy to get free.
- But silicon is mostly use bcz, Ge get unstable at high temperature.
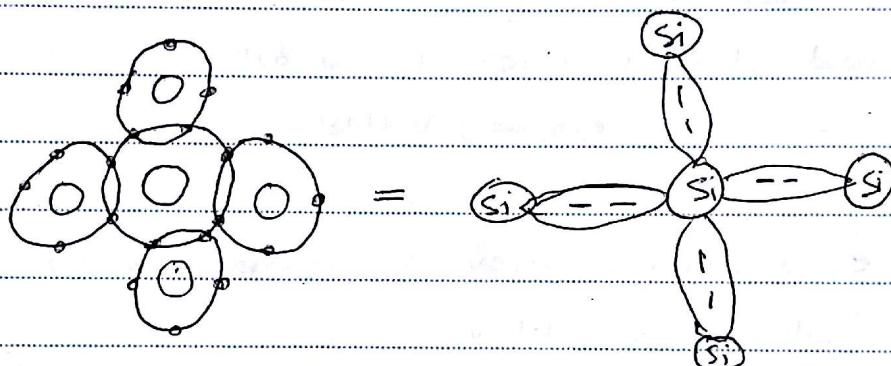
### 3 Silicon Crystal.

- Silicon crystal is formed, by the sharing the valence electrons (4) with adjacent 4 silicon atoms.




- crystal is  
a material  
having solid  
& fixed structure


Si crystal.
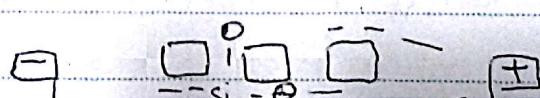
### 4 Types of Current flow.

- At room temp.: no. of electrons moves from Valence band to Conduction band becomes free electron & leaves Vacancy. = hole.
- Deficiency cause hole, that is left due to electron escape.
- Electron & Hole current  
When voltage is applied to intrinsic semi-conductr. free electrons will move toward the +ve terminal. & this flow is called electron current.



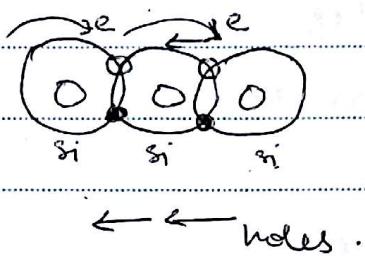- Hole current is caused, when electron escapes the valence band/shell, so holes is replace and moves on.



## 5. Intrinsinc Semi-conductor.

- Semi-conductor that is all pure is called Intrinsinc semi-conductor.

Carbon, Silicon & Germanium.

## 6. Doping.

- Doping is the process of adding impurities to the pure semi-conductor for increasing the number of current carriers (electron (holes)).

## 7. Extrinsic Semiconductor.


### n-type & p-type semi-conductors.

#### - n-type E. semi conductor.

- n-type semi-conductor is formed by adding pentavalent atoms impurities to the pure silicon.


-- These atoms have 5 valence electron. Arsenic (As), Phosphorus (P), Antimony (Sb).

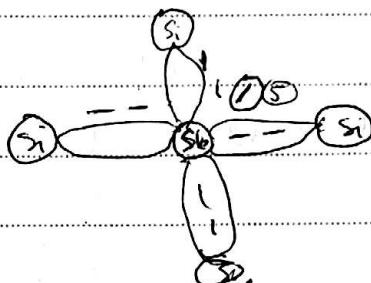- majority carriers are electrons, holes in minority carrier.


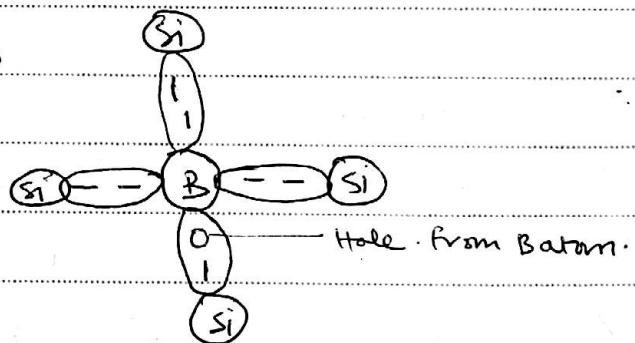
### P-type - Semi-conductor.

- P-type semi-conductor is formed by adding tivalent atoms impurities to pure silicon.
- 3 valence electron, Boron(B), Indium, Gallium(Ga)
- majority carriers are holes & minority are electrons.



### Extra

### Electric current

Electric current is the flow of electrons in the medium,  $I = q/t$

### Potential Difference

Energy dissipated in moving charge from one point to another.  $P.D = \frac{\text{Work done / energy}}{\text{charge}}$ .

### Resistance

The friction offered to the flow of current.

$$R = (\text{const}) V/I \quad R \propto V, R \propto 1/I$$

## Unbiase Diode / Diode .

- Silicon block doped with Pentavalent impurity & other part with trivalent impurity , forming pn junction and called as basic Diode. (Pn-junction allow  $\rightarrow$  one direction flow.  $\textcircled{5}$  devices to work.)
- **P-type material** (Pentavalent atom + Silicon atom , majority carriers electrons.)
- **n-type material** (trivalent  $\textcircled{2}$  atom + silicon atom , majority carriers holes).
- "Depletion region forms , free electrons moves in P-region, leaving Pentavalent ions, Holes moves toward n-region leaving trivalent ions  $\ominus$  "
- Depletion refers to the region its neither have free electrons / holes.
- Potential Barrier is created and no further electrons can move into P-region. which then needs external voltage source, to cross the barrier,  $S_i = 0.7V$ . P.D  $E_{be} = 0.3V$  P.P.  $25^\circ C$ .
- Depletion Region is thin layer of +ve & -ve ions. / called as Pn-junction as well." The region is depleted of charges (electrons / holes). It contains the Pentavalent and trivalent ions.

## Biassing Diode.

As no more electrons could flow across the depletion-region, so external source is required for which Biassing is require. we use generally a dc voltage source for electronic device to work.

- bias refers to establish dc source/ across the electronic device operating conditions
- Forward Bias.
- Reverse Bias.

## 2- Forward Bias.

- Bias to apply DC Source.
- Forward Bias is condition to allows current through Pn-junction.

- negative side to n-type
- +ve side to p-type.

- The  $V_{bias}$  is more than


Barrier potential so cross

the barrier & flow of electrons, starts

- +ve side of terminal attracts the electron, where path is provided by holes.

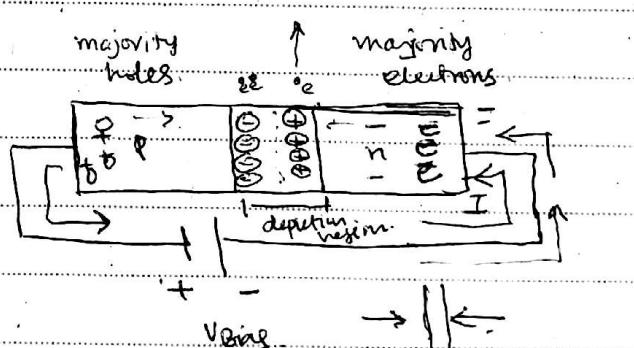
## Effect on Depletion Region.

As more electrons flow, into depletion region the positive ions reduced, as more holes flow into depletion region from other side -ve ions reduced, so depletion region gets narrower / shrinks



$\therefore$  current  
 $P \leftarrow N$

$(+)$  direction

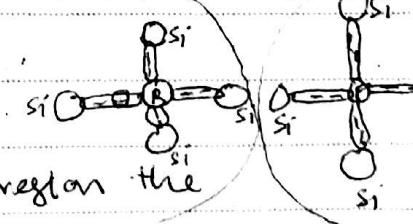

### 3. Reverse Bias.

- Reverse Bias is the condition, which ~~opposite~~ prevents current through Diode.

Current through Diode

⇒ -ve side of  $V_{bias}$  to P-type

⇒ +ve side of  $V_{bias}$  to n-type.

Effect on depletion region.

When current start to flow,

- +ve side Bias attracts -ve free electrons / pentavalent electron.

so more +ve pentavalent ions


creat.

- -ve side Bias attracts +ve holes,

so electrons get transferred and trivalent +ve ions are formed.

which makes depletion region

more WIDER.

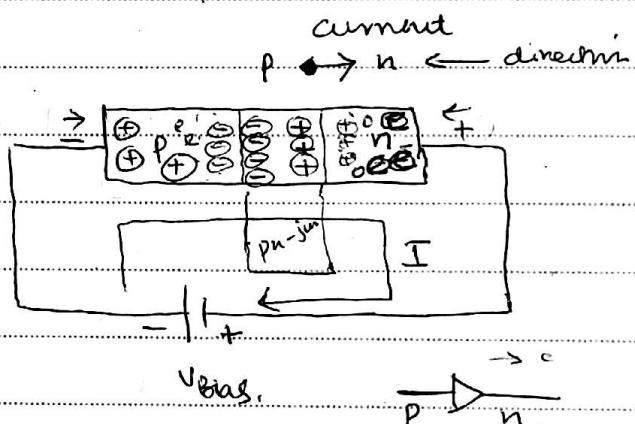

- Current is due to flow of minority carriers in Reverse-Bias.

- Reverse current flows due to minority carrier in n & p type material.

~~n-holes/p-electrons~~

- free minority electrons in P-region is pushed by -ve Bias voltage, it cross the barrier, combines with minority holes in n-region & flows down to +ve terminal of battery causing very small reverse current.

#### 4. Reverse Breakdown


- When reverse Bias voltage is increased gradually current will also increase & change drastically.

(breakdown voltage)

- So free electron (minority) in P-region ; as it's with high speed so collide with the O<sup>-</sup> terminal of other valence electrons, and this number increases,
- It then cross the barriers, where on other side there is already <sup>n-region</sup> where these majority electrons, ~~is~~ current will increase with very high intensity, so high reverse current is generated that can damage the diode / device.


- When the reverse bias voltage is increased to breakdown voltage, the battery pushes  $e^-$  (minority carriers of P-type) into the n-type, electrons on their way known as resulting in Large current, Known as Breakdown.

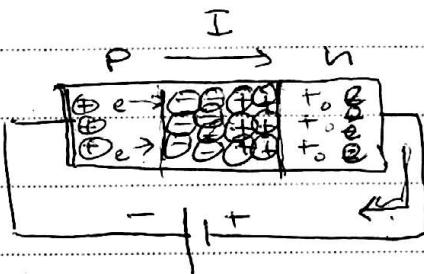- V "The external reverse bias voltage when increases to a value called breakdown voltage, reverse current will increase drastically" and could damage the diode."


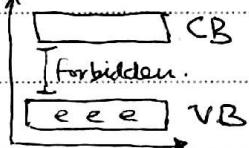
## 1- Energy Levels. (already discussed)...

- Electrons revolve around the nucleus in permitted energy levels, contributing to the energy of that shell. <sup>even</sup>
- Valence Band. - Forbidden Region.
- Conduction Band.




## 2- Barrier Potential.

$\rightarrow I$  con-current.

- After formation of Pn-junction electrons diffuse into the P-region & holes diffuse into n-region near by junction.

Leaving  $\oplus$  and  $\ominus$  ions.

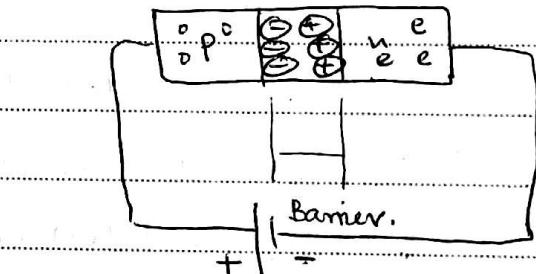


\* The barrier potential

- A point is reached when. depends upon the total charge of electrons/holes. Several factors. opposes the further diffusion, & equilibrium is reached.
  - Barrier is created as because of  $\oplus$  and  $\ominus$  charges in the depletion region and electric field is created.
  - "The energy require to move an electron through depletion region into p-region is called Barrier-Potential."
- \* Semiconductor material
  - \* amount of Doping
  - \* and temperature

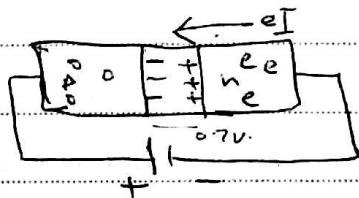
### 3. Energy Hill

Energy Hill is the barrier / energy gradient across the depletion region <sup>n-type</sup> electron must climb to get into P-region.


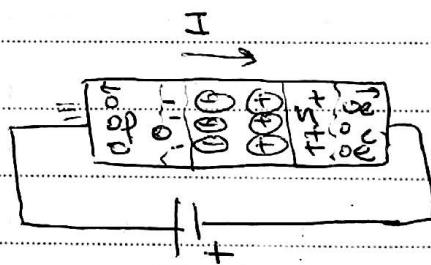
### 4. Reverse Bias Diode

- Reverse Bias is the condition where current is experiencing huge resistance.



- +ve terminal is connected to n-type & -ve terminal to the P-type part of the diode.

o electrons in P-region are forced by +ve voltage source to

- As the +ve terminal attracts the electrons from n-type region more +ve ions will produce & increases. On other side -ve terminal electrons flows through holes and increases -ve ions near junction which causes widening of depletion region.

cross depletion region and combine with minority holes in n-region produces V. low reverse current

- At a stage, Reverse current is produced as electrons of -ve terminal forces minority carrier in P-region to cross depletion and enter in P-region.

## Lectures .

I- Basic Ideas (Diode)

(week-4)

- A diode is a single Pn-junction device, part of the diode is n-type semi-conductor and part of it is p-type semi-conductor.
- Diode is a non-linear device, because of its potential barrier due to which it behaves non-linearly.

→ below knee.

V - small.

I - small.


→ above knee

V - exceeds.


I - huge change.

Symbols for Diode :

- P-side of diode is called anode & n side is called cathode. Diode symbol looks like an arrow that points from P to n side of the diode.

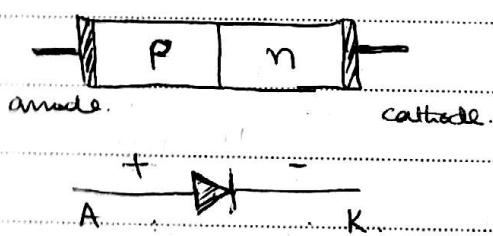 $\vec{I}_D$  (conventional).

(a)

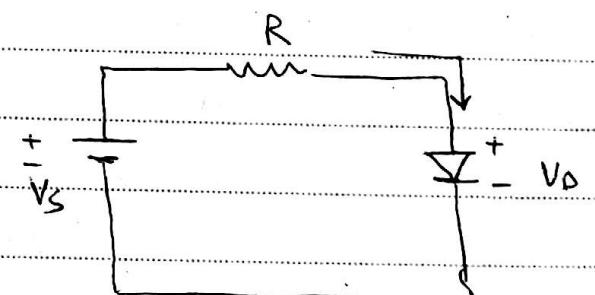


(b)

- Diode is like a switch. It's closed (ON) when it's in forward bias mode and open (OFF) when it's in reverse bias mode.

 $\rightarrow \circlearrowleft$ Reverse  
Bias $\rightarrow \circlearrowright$ Forward  
Bias.
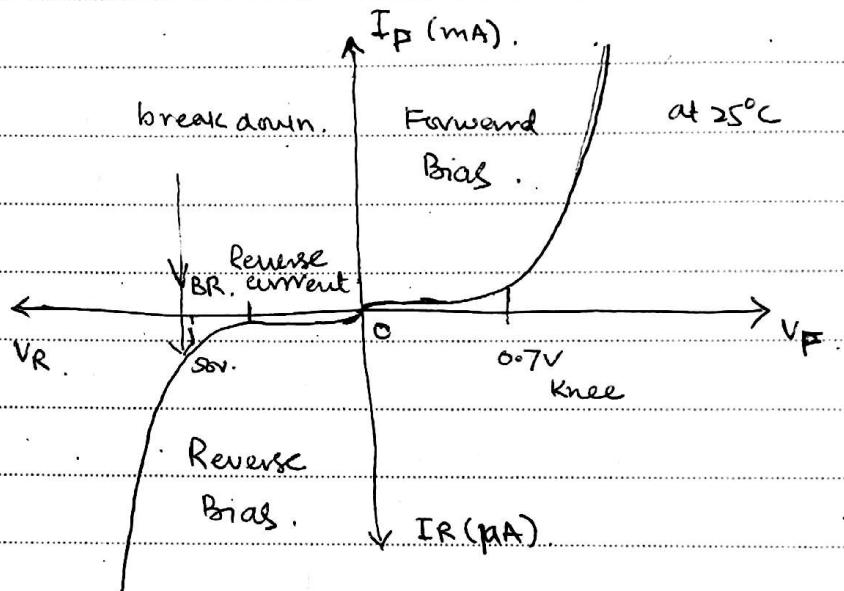
## V-I Characteristic Curve of Diode

- above the knee in forward bias current increase rapidly.



- In reverse bias there is a small reverse current, due to minority carriers until the breakdown stage reaches.

### Power Dissipation.

- Power dissipation is calculated in same way as that of resistor.

$$P_D = V_D I_P \text{ (watts)}$$

dissipation = release / emits

- Power rating is the maximum power that the diode can safely dissipate without degrading its properties.

$$P_{max} = V_{max} I_{max.} \text{ (watts)}$$




Visit [tshahab.blogspot.com](http://tshahab.blogspot.com) for more.

## 2- Ideal Diode / First Approximation

- ideal-diode acts like a switch, it's closed (on) in forward bias mode and open (off) in reverse bias mode.

- The equivalent circuit for 1 diode is

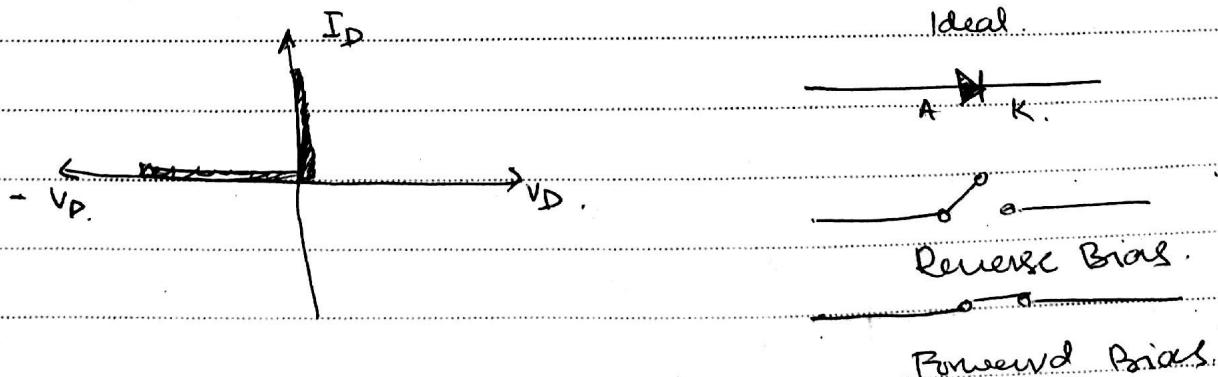


### 3- The Second Approximation


In Second approximation, diode as switch and 2<sup>nd</sup> factor, barrier potential is added to it.

- The 2<sup>nd</sup> approximation give more accurate results for load current and voltage.

Circuit (equivalent)

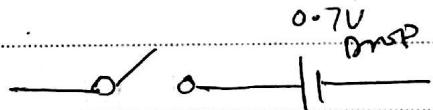

Reverse Bias

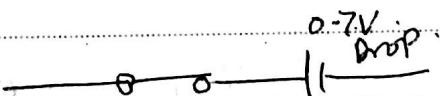

Forward Bias

## 7- Load Lines

Load line is used to calculate the exact current and voltage of Diode.

### Equation for Load line

The current through diode is

$$I_D' = \frac{V_S - V_D}{R_S} \quad \text{--- (7.1)}$$


Current remains same, as it series circuit.

Equation 7.1, is a linear so give us a

straight line, on the graph for  $V$  &  $I$

- Example to explain

Load line

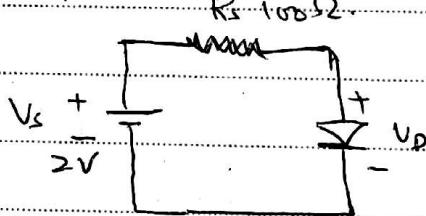


For  $V_s = 2V$ ,  $R_s = 100\Omega$ .

Load current will be

$$I_D = \frac{2 - V_D}{100}$$

(i)- Let  $V_D = 0$ .

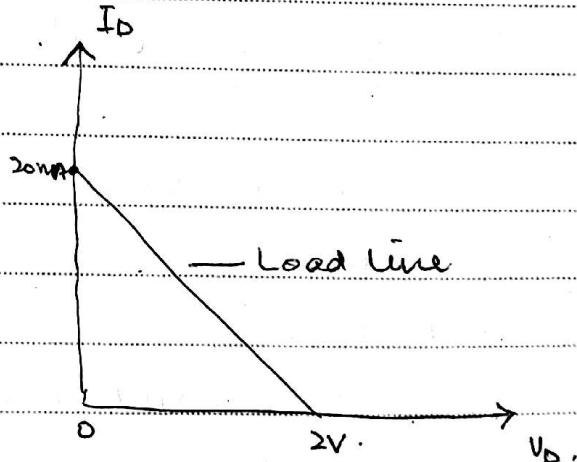

$$I_D = \frac{2V - 0}{100\Omega} = 20\text{mA} \quad (\text{saturation point})$$

(ii)- it gives one point. now assume  $V_D = 2V$ .

$$I_D = \frac{2V - 2V}{100} = 0A \quad (\text{cutoff point})$$

it gives another point, to be drawn at graph.


## The Q-Point

- The point of intersection of diode curve and load line is known as Q-point. abbreviated for quiescent which means "at rest".

Q-point is operating point of the diode in this example. Q-point has values of

$$I_D = 12.5 \text{ mA} \text{ and } V_D = 0.75 \text{ V}$$

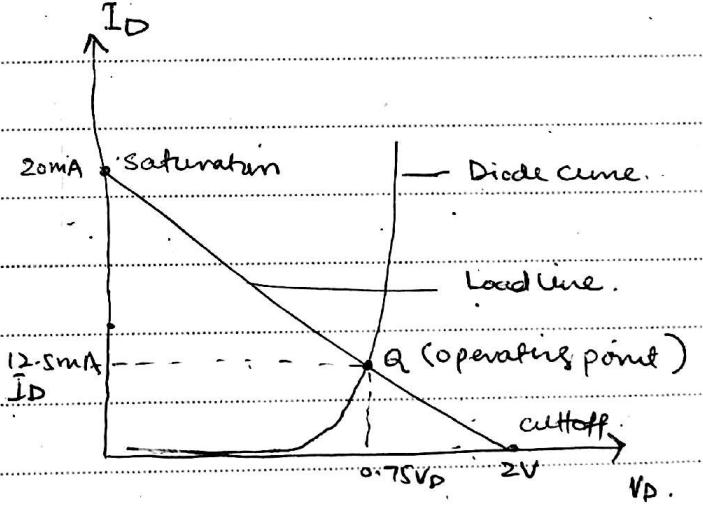- So the current & voltage of diode satisfy both Ohm's Law & diode curve.



# [Diode - Applications]

(Lectures.)

## Rectifiers.

Week-5

Most electronic devices use dc-voltage to work, since power-line voltage is ac-voltage, so the first thing is to convert ac-voltage to dc-voltage, that is provided by the power supply of the device, and the circuit that produce dc-voltage is called Rectifier.

- The circuit that convert ac-voltage to dc-voltage is called Rectifier.


### I- Half-Wave Rectifier

In the Half-wave rectifier, the diode is conducting during <sup>positive</sup> half the cycle, as the diode is "on" and in forward bias, whereas in negative half cycle diode is "OFF" as it's in reverse bias, so it's in non-conduction state.

- This half-wave voltage produces a unidirectional load current.
- For ideal diode, the peak output voltage equals the peak input voltage.

$$\text{Ideal half wave: } V_p(\text{out}) = V_p(\text{in}).$$
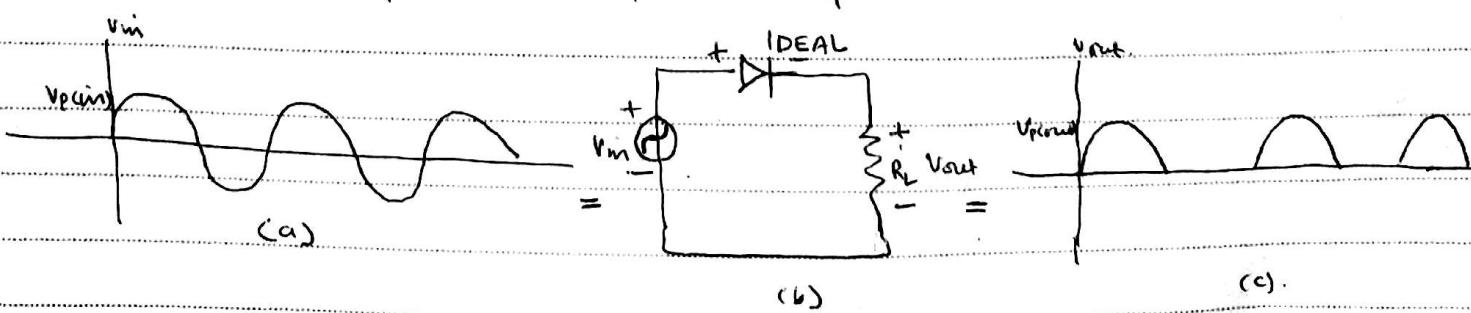
$$V_{\text{rms}} = \frac{V_p}{\sqrt{2}}$$



Dated :

### - DC-Value of Half-wave Signal :

The dc value is the average value of the signal.

The dc value for half wave signal is ;

$$V_{avg} = V_{dc} = \frac{V_p}{\pi}$$

" area under  
the curve .



$$V_{dc} = 0.318 V_p.$$

So  $V_{avg}$  is the 31.8 percent of the peak value of the voltage.

### - Output Frequency :

Each <sup>+ve half</sup> cycle of input voltage produces one <sup>half-</sup> cycle of output voltage so ;

$$\text{Half wave : } f_{(out)} = f_{(in)}$$

### - For Second Approximation :

In 2nd. Approximation, the input voltage source must use voltage to cross- the barrier-potential of  $0.7V$ , so the  $V_{out}$  will be ;

$$\text{2d half wave : } V_{p(out)} = V_{p(in)} - 0.7V.$$

### 3- Full-Wave Rectifier.

- A full wave rectifier allows unidirectional current through the load during the entire input cycle, thus changing ac-voltage to dc-voltage.


- The full wave rectifier is equivalent to two half wave rectifiers

Each of these rectifiers has an input voltage equal to half of the Secondary Voltage.


Diode  $D_1$  conducts on the positive half cycle,

Producing positive load voltage, and Diode  $D_2$  conducts on the negative half cycle, producing  $\ominus$ ve Load voltage,

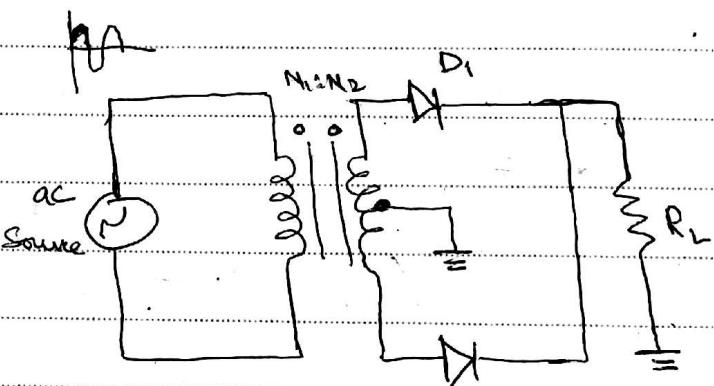
So as a result rectified load current flows during both half cycles.




Full-wave Rectifier (a)

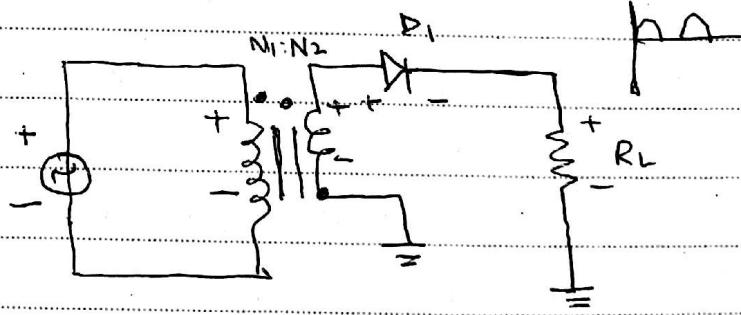

$\oplus$ ve half cycle circuit (b)

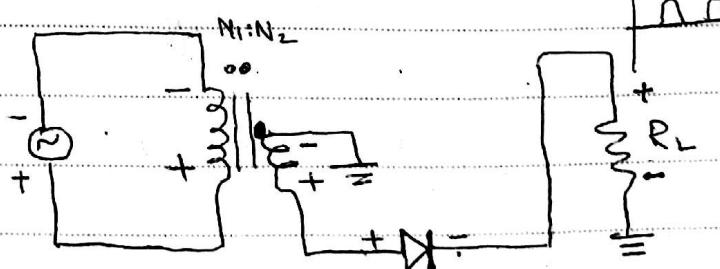

$\ominus$ ve half cycle circuit (c)

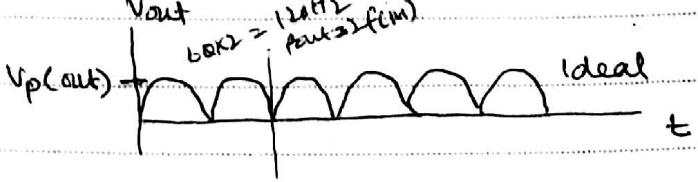

Full-wave output (d)

Dated : \_\_\_\_\_

- Dc or Average value for Full wave rectifier.

Since the full wave rectifier has twice as many positive cycles as that of half wave,

So  $V_{avg}$  is ;

$$V_{rms} = \frac{1}{\sqrt{2}} V_p$$

$$V_{avg} = V_{dc} = 2 V_p / \pi \quad 2/\pi = 0.636 \text{ or } 63.6\%$$

So the average value is 63.6% of the peak value.

- Output Frequency.

Same as it has twice as many positive cycles compare to half wave so its frequency is

$$T_m = \frac{1}{60Hz} 16.7ms. \quad (\text{HW})$$

$$\text{Full wave } f_{out} = 2 f_{in}.$$

$$T_{out} = 0.5(16.7) (\text{HW}) \\ = 8.33 \text{ msec.}$$

- Second Approximation.

As full wave rectifier is equivalent to two half wave rectifiers. So peak output voltage is

∴ For ideal.


$$V_{p(out)} = V_{p(half)} - 0.7V$$

$$V_{p(out)} = \frac{1}{2} V_{p(in)} - 0.7V$$


$$V_{p(out)} = \frac{1}{2} V_{p(see)} - 0.7V.$$

Dated : \_\_\_\_\_

## Power Supply Block Diagram

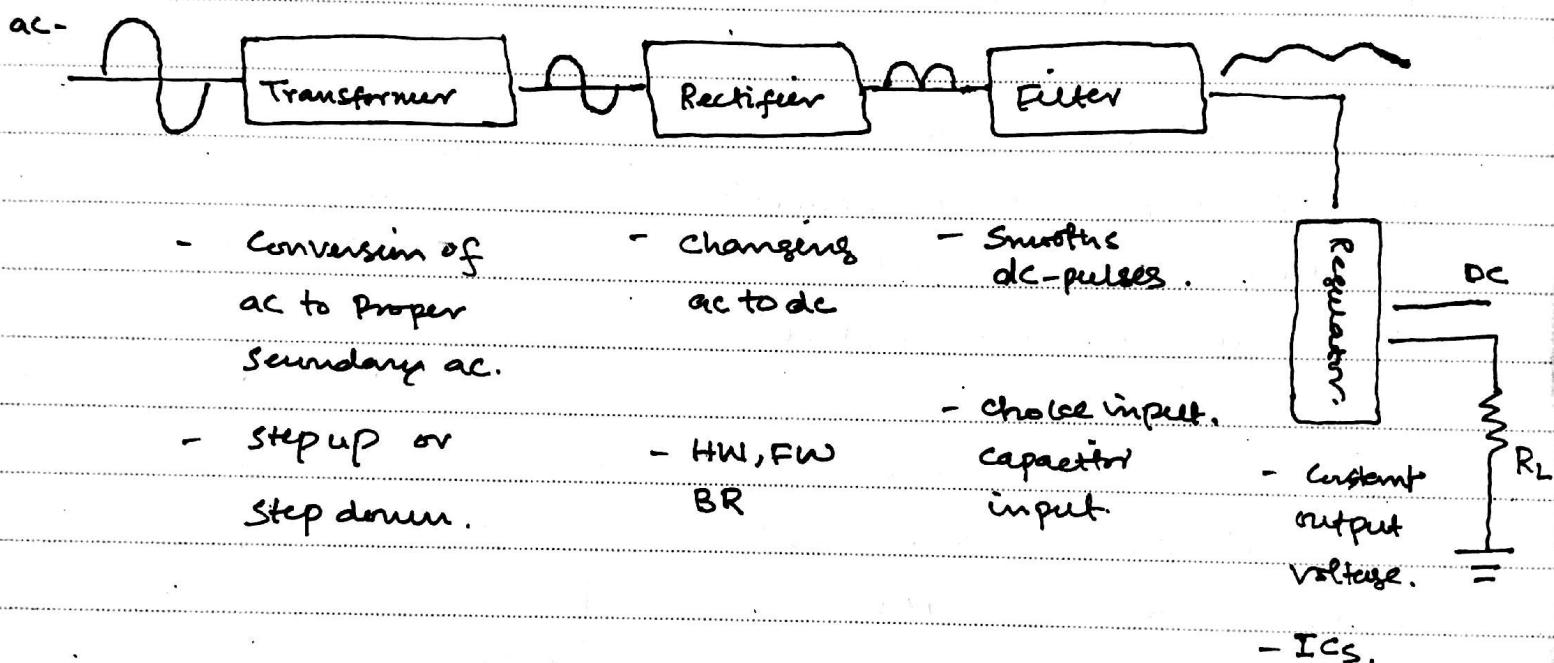

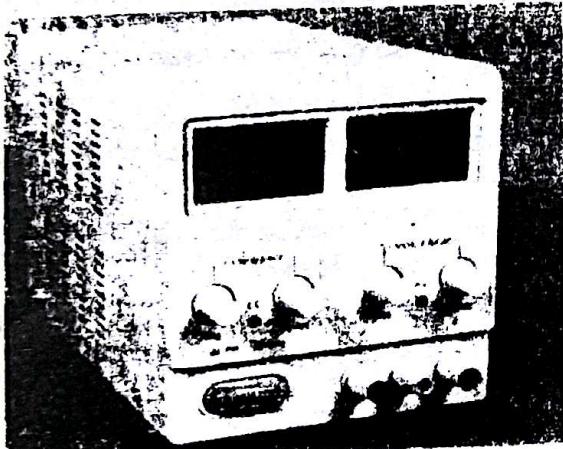Visit [tshahab.blogspot.com](http://tshahab.blogspot.com) for more.



# DC Power Supplies

## 17.1. Introduction

**M**ost of the electronic devices and circuits require a dc source for their operation. Dry cells and batteries are one form of dc source. They have the advantage of being portable and ripple-free. However, their voltages are low, they need frequent replacement and are expensive as compared to conventional dc power supplies. Since the most convenient and economical source of power is the domestic ac supply, it is advantageous to convert this alternating voltage (usually, 220 V rms) to dc voltage (usually smaller in value). This process of converting ac voltage into dc voltage is called *rectification* and is accomplished with the help of

- (i) rectifier,
- (ii) filter; and
- (iii) voltage regulator circuits.

These elements put together constitute dc power supply.

## 17.2. Unregulated Power Supply

An unregulated power supply is one whose dc terminal voltage is affected significantly by the amount of load. As the load draws more current, the dc terminal voltage becomes less.

## 17.3. Regulated Power Supply

It is that dc power supply whose terminal voltage remains almost constant regardless of the amount of current

1. Unregulated Power Supply
2. Regulated Power Supply
3. Steady and Pulsating DC Voltages
4. Rectifiers
5. Full-wave Bridge Rectifier
6. Filters
7. Bleeder Resistor
8. Voltage Regulation
9. Zener Diode Shunt Regulator
10. Voltage Dividers
11. Complete Power Supply
12. Voltage Multipliers
13. Half-wave Voltage Doubler
14. Full-wave Voltage Doubler
15. Troubleshooting Power Supplies
16. Controlled Rectification
17. Silicon Controlled Rectifier (SCR)
18. UJT Controlled Circuit

from it. An unregulated supply can be converted into a regulated power supply by adding a voltage regulating circuit to it (Art. 17.17).

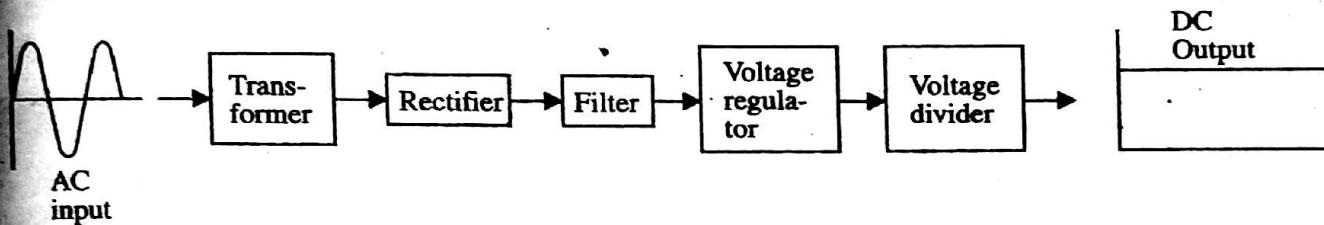


Fig. 17.1

A typical dc power supply consists of five stages as shown in Fig. 17.1.

### 1. Transformer

Its job is either to step up or (mostly) step down the ac supply voltage to suit the requirement of the solid-state electronic devices and circuits fed by the dc power supply. It also provides isolation from the supply line—an important safety consideration.

### 2. Rectifier

It is a circuit which employs one or more diodes to convert ac voltage into pulsating dc voltage.

### 3. Filter

The function of this circuit element is to remove the fluctuations or pulsations (called ripples) present in the output voltage supplied by the rectifier. Of course, no filter can, in practice, give an output voltage as ripple-free as that of a dc battery, but it approaches it so closely that the power supply performs as well.

### 4. Voltage Regulator

Its main function is to keep the terminal voltage of the dc supply constant even when

- (i) ac input to the transformer varies (deviations from 220 V are common) or
- (ii) the load varies.

Usually, Zener diodes and transistors are used for voltage regulation purposes. Again, it is impossible to get 100% constant voltage but minor variations are acceptable for most of the jobs.

### 5. Voltage Divider

Its function is to provide different dc voltages needed by different electronic circuits. It consists of a number of resistors connected in series across the output terminals of the voltage regulator. Obviously, it eliminates the necessity of providing separate dc power supplies to different electronic circuits working on different dc levels.

### Comments

Strictly speaking, all that is really required for conversion from ac to dc is a transformer and rectifier (in fact, even the transformer could be eliminated if no voltage transformation is required). The filter, voltage regulator and voltage divider are mere refinements of a dc power supply though they are essential for most applications except for battery charging and running small dc motors etc.



## 2- Clippers and Limiters.

### Clipper:

A Clipper is a circuit that either removes positive or negative part of the signal. It basically shapes the signal to the required conditions.
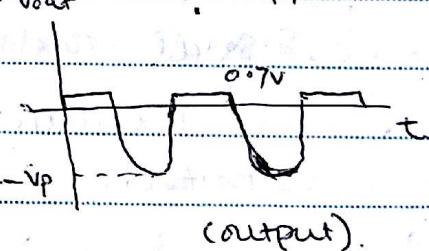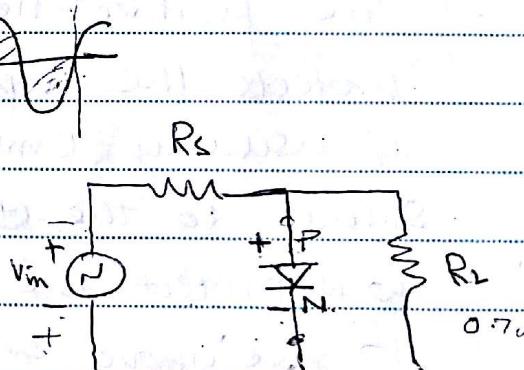
#### Positive Clipper :



During the +ve half cycle the diode is turned on and the looks like a short across the output terminal, only  $0.7V$ , will appear in the +ve half cycle and during the negative half cycle diode acts like open and all the negative voltage appear across the Load resistor.


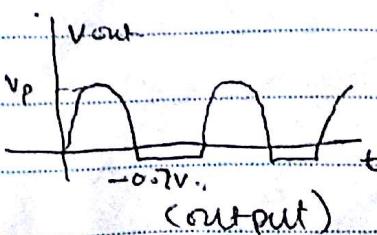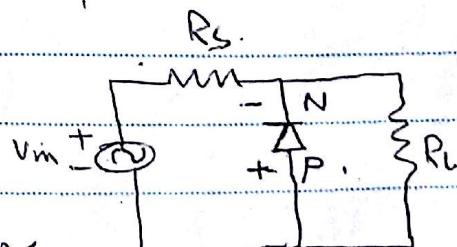
#### Negative Clipper :


By reversing the polarity of the diode, we get a negative clipper.

For the +ve half cycle, the diode would be off and voltage will appear across the load, whereas for the -ve half cycle the diode will conduct and  $0.7V$  will appear through the -ve half cycle.


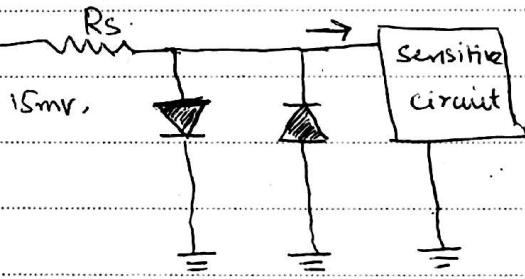
## Limiter

- A Limiter is circuit that prevents input voltage from undesirable increase for sensitive circuits.
- The positive-negative Limiter protects the input signal, if usually  $15mV$  is an input signal so the  $\oplus$ ve limiter will protect the input signal to rise above  $0.7V$ . and the  $\ominus$ ve limiter will protect the signal to drop below  $-0.7V$ . so the variation to input is limited.



- For normal operation both diodes would be OFF.

### 3. Clamper

The Clamper is a circuit that shifts a signal positively or negatively by adding the dc-component voltage to the signal.  $\oplus$ ve DC is added.

#### - Positive Clamper

Positive Clamper basically shifts the signal  $\oplus$ vely upwards, by adding the dc-voltage.

For the first  $\ominus$ ve half cycle, the diode is



forward bias, and capacitor starts charging upto the level of  $V_p - 0.7V$  approx. after the quarter  $\oplus$ ve half cycle, the diode starts to reverse bias, as because of the polarities, so the voltage will appear across the load-resistor upto the value of  $2V_p$  approx.  $\therefore$

$V_{P(in)} - 0.7$ ,  $2V_p = ac + dc$
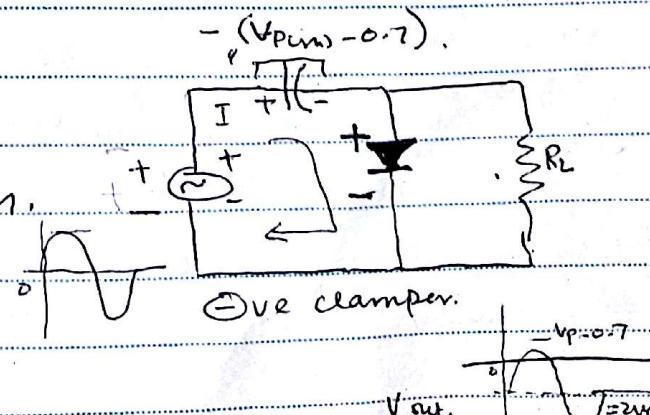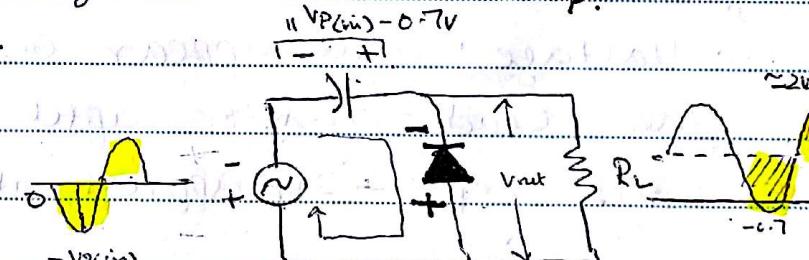
#### - Negative Clamper

Negative Clamper shifts the signal  $\ominus$ vely downwards by

changing the diode direction, which changes capacitor polarities as well.



Dated :

Over DC-added.

Over 4-cycle =

$$V_{pin} - V_{pin} + 0.7 = 0.7$$

Over 1/4 cycle =

$$-V_{pin}, -V_{pin} + 0.7 = -2V_p$$

For the positive half cycle the diode is forward bias and the capacitor is charging upto the level of  $-(V_{pin} + 0.7)$ . After

the quarter Over half-cycle


the diode starts to reverse bias

as because polarities, so the

Voltage will appear across

the load-resistor upto the

level of  $-2V_p$  approximately

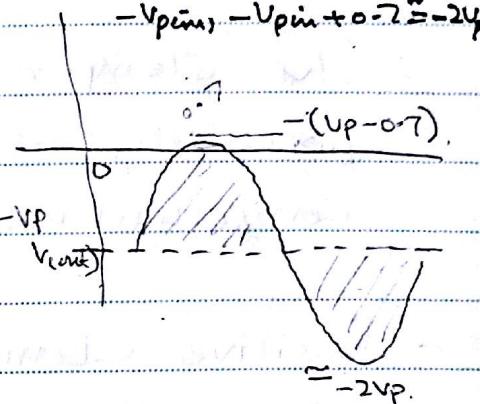

Over clumper

output.

- Over dc-value is added.

Clampers are used in television receivers, radars and communication systems as well.


Dated: \_\_\_\_\_

(Lectures)
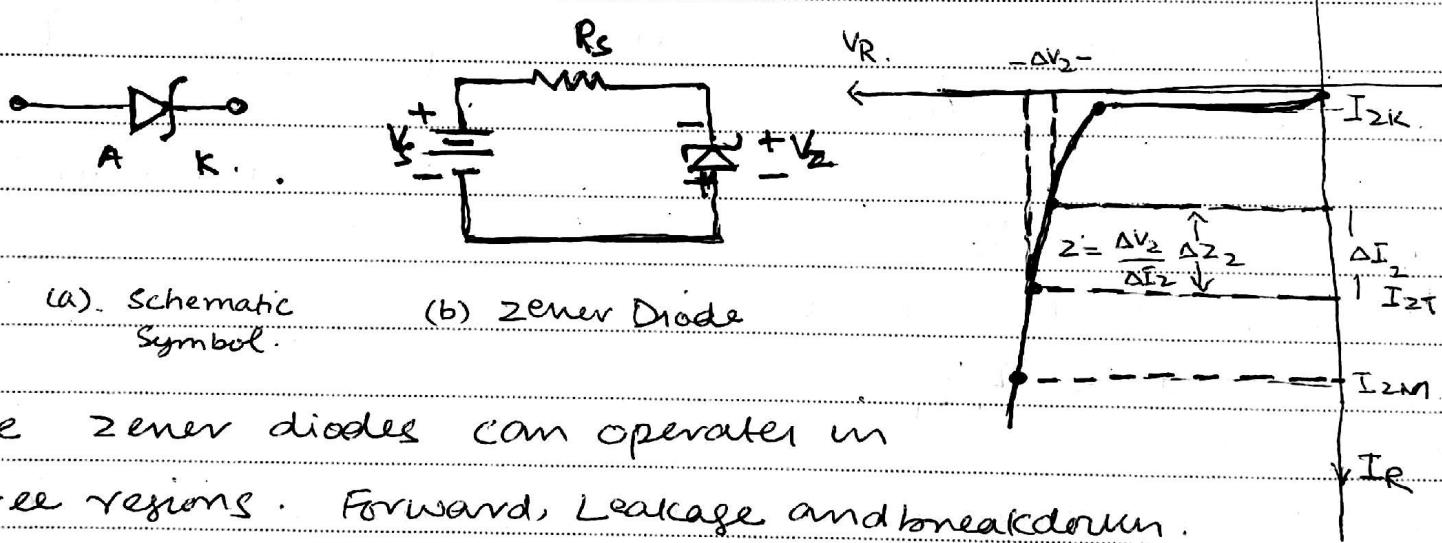
## 1. Zener Diodes.

Week-(7+8)

- A zener diode is a silicon Pn-junction device that is designed to operate in the reverse breakdown-region. The zener diode is a backbone for voltage regulator circuits which provides the constant voltage despite large changes in Line Voltage.
- Zener diodes equivalent circuit



- The zener diodes can operate in three regions. Forward, Leakage and breakdown.
  - In forward region it starts conducting [V-I-characteristic] from 0.7V, just like silicon diode.
  - In leakage region (between 0 - breakdown) it has only small reverse current.
  - In breakdown region, the current has increased sharply, whereas the voltage remains constant approximately equal to  $V_z$ .

When breakdown voltage is greater than 5V, Avalanche effect is produced, (large reverse current because of minority carriers, and when  $V_{BR} < 5V$ , Zener effect is produced).

# Bipolar Junction Transistors (BJTs)


(Lectures)

## I- The unbiased Transistor / BJTs.

Week - 9.

- BJTs stands for Bipolar Junction transistor, bipolar means using both polarities (electrons & holes)

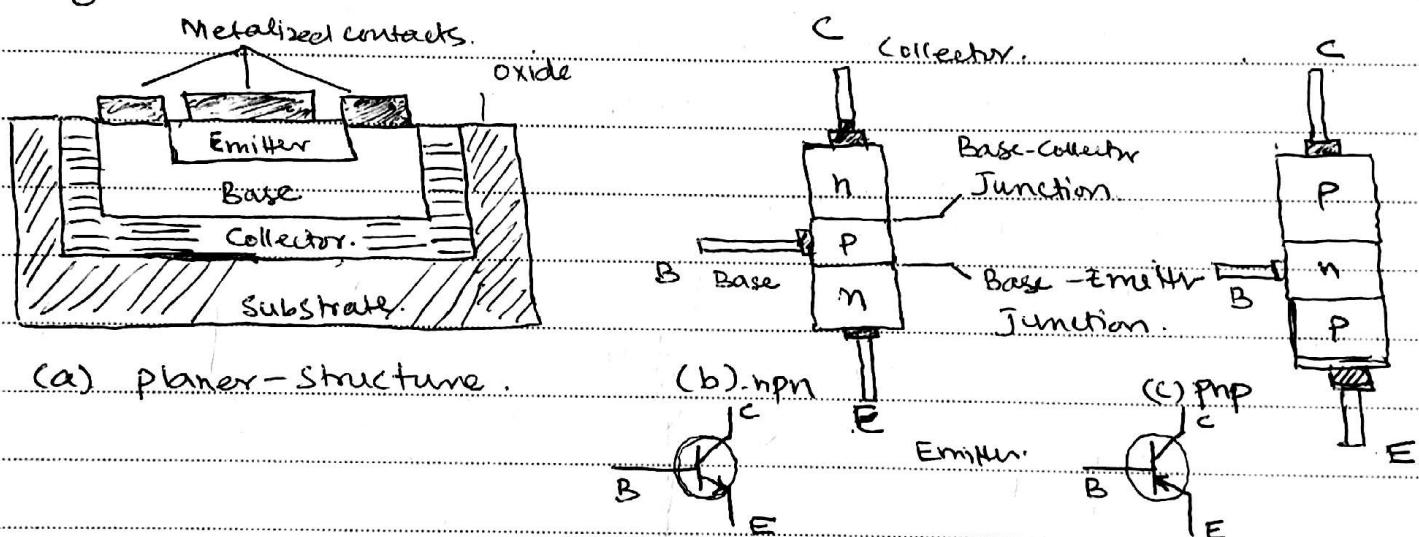Transistors are formed by the formation of three regions emitter, base & collector separated by two pn-junctions.




- BJTs have two types, npn & pnp transistors.  
 npn has two n-regions and one p-region whereas pnp has two p-regions and one n-region separated by two pn-junctions. pn-junction joining Base and emitter region is called as Base-Emitter junction and pn-junction joining Base and collector is called as Base-Collector junction.  
 The emitter is the bottom region doped heavily, the central region doped lightly and collector is the top-region doped moderately.

Transistors are used for amplification purposes, and could be used as a switch as well.
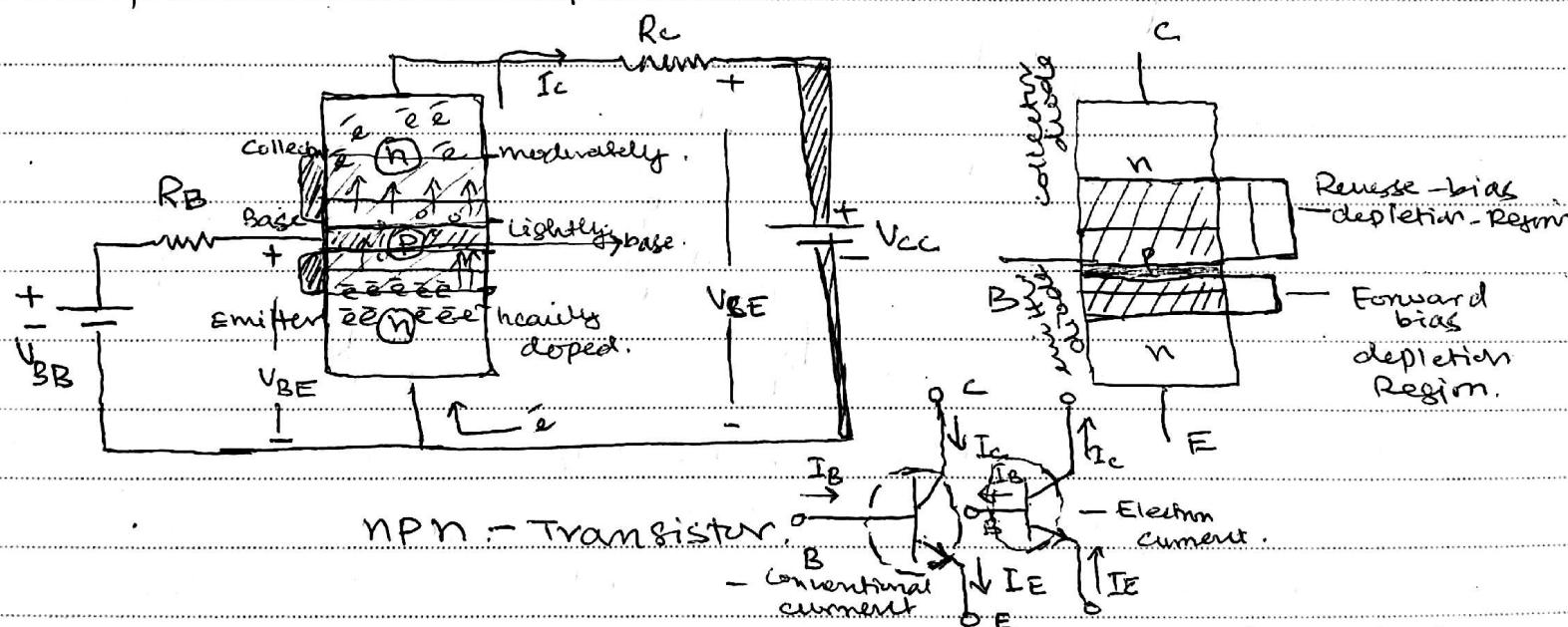
## 2- Biased-Transistor / Transistor Operation :

For the transistor to run properly both the p-n-junction should be biased properly with external dc - voltage sources . correctly

For both transistor n-p-n or p-n-p base-emitter (BE) junction should be forward-bias and base-collector (BC)-junction should be reverse bias . the operation of both n-p-n & p-n-p are same .



The Forward-bias Base-Emitter narrows the BE-depletion region , whereas reverse-bias base-Collector widens BC the depletion region . As the  $V_{BB}$  forward bias the emitter-region , it forces the free electrons to cross the depletion region and enter into the Base . The thin base gives almost all the electrons (es) enough time to diffuse into the Collector , where these electrons are pulled by the +ve terminal of the  $V_{CC}$  voltage producing collector-current ( $I_C$ ) .

### 3- Transistor Currents

- Transistor contains three currents, emitter current ( $I_E$ ), base current ( $I_B$ ) and collector current ( $I_C$ ).  
 As the emitter is the source of electrons so  $I_E$  is the largest current, the base current is much small, whereas all the electrons pass to collector from base (approximately) so collector current is almost as large as emitter.

For currents relationship


apply Kirchhoff's current law: so

$$I_E = I_C + I_B$$

emitter current is sum of

base current & collector current. (a). n-p-n-

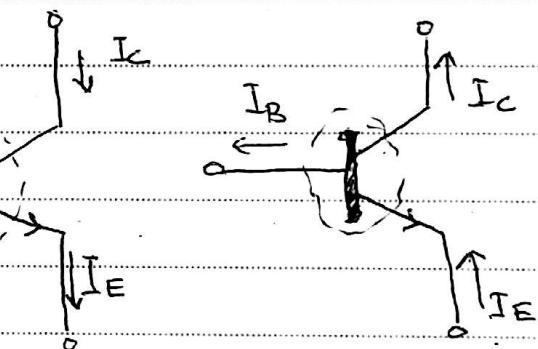and  $I_C \approx I_E$   $\because I_B$  is much smaller.  
2% of  $I_C$ .



Conventional current.

(b). n-p-n-  
electron current.

**Alpha :** The dc-alpha ( $\alpha_{dc}$ ) is the ratio of collector current to the emitter current. the ratio is always less than 1, as  $I_C$  is approximately equal to  $I_E$ .

$$\alpha_{dc} = I_C/I_E$$

**Beta :** The dc-beta ( $\beta_{dc}$ ) is the ratio of collector current to the base current. It's called as Current gain, because smaller base-current controls larger collector current.

Its values lies between 100 & 300. (power transistor) &

$$20\text{ to }150 \text{ (For H. power transistor). So, } \beta_{dc} = \frac{I_C}{I_B}$$

### 3- Collector Curves.

The collector curve is between  $V_{CE}$  (Collector-Emitter voltage) and collector current ( $I_C$ ) for the fixed value of base current ( $I_B$ ).

Collector voltages and powers,

using Kirchhoff's Voltage Law in the collector loop we gets;

$$V_{CC} = V_{CE} + I_C R_C$$

$$\& P_D = V_{CE} I_C$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$I_C = \frac{V_{CC} - V_{CE}}{R_C}$$

Region of Operations:



Transistor operates in different region depends upon its usage.

As an amplifier transistor is operated in Active-region.

In active/Linear Region emitter diode is Forward-bias and collector diode is reverse bias, where as

the collector current remains constant, because it gather almost all electrons that emitter injects in the base so its not effected by voltage of collector.

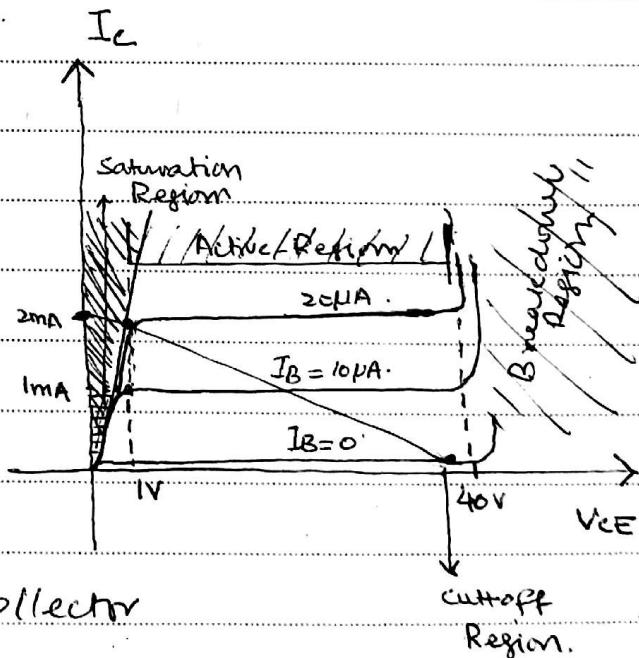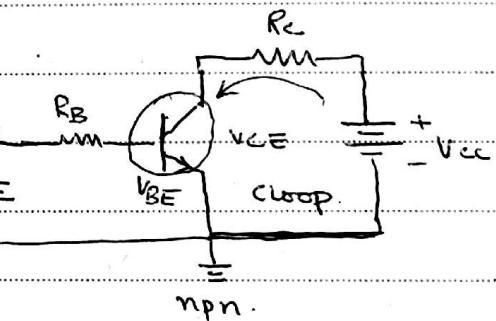Second one region is breakdown-region. Transistor is not optimized for breakdown region, so it would be damage if its operated in breakdown region.





Visit [tshahab.blogspot.com](http://tshahab.blogspot.com) for more.

Dated : \_\_\_\_\_

Saturation - Region and cutoff - region are the operated region when transistor is use as a switch:

In Saturation-region both emitter and collector diodes are forward bias, as collector is yet not get reverse-bias, so here is a sharp rise in the collector current  $I_c$ . Saturation-region resembles Switch ON.

In cutoff region, both emitter and collector are reverse bias, so there is a small reverse collector current that flow in reverse direction, where as base-current is zero. Cutoff region resembles Switch OFF.

$$\begin{array}{l} I_{c(sat)} = \text{max.} \\ V_{CE} = \text{min}(0) \end{array}$$

$$I_c = \text{min}(0).$$

$$V_{CE} = \text{max}(V_{cc}).$$

## 2- The Load Line


The load line is effect of load on  $I_C$  and  $V_{CE}$ .

The straight line between the  $I_C$  and  $V_{CE}$  gives the load line.

Load line equation is given by:

$$V_{CE} = V_{CC} - I_C R_C \quad \text{---(1)}$$


$$I_C = \frac{V_{CC} - V_{CE}}{R_C}$$

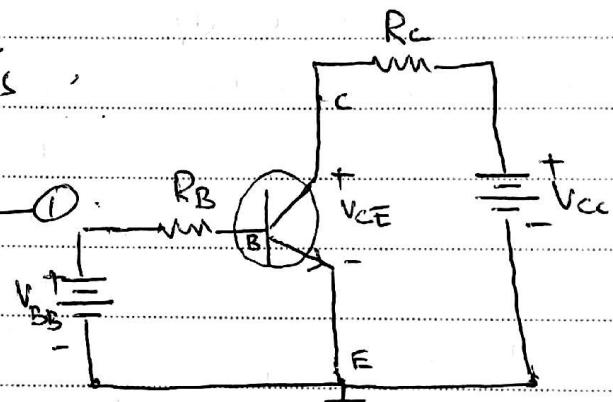

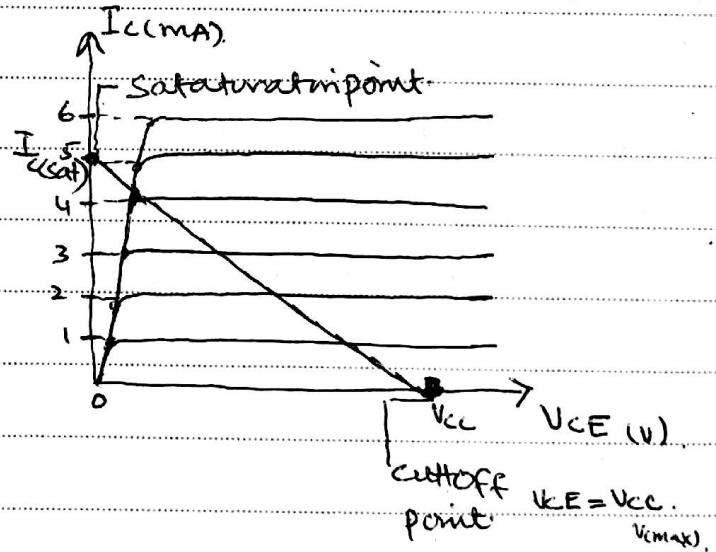(a) - Common Emitter (npn).

Saturation point is the point where  $V_{CE}$  is approximately zero and collector current is maximum, so it's given by.

$$I_{C(sat)} = \frac{V_{CC}}{R_C}, \quad V_{CE} = 0.$$





Cutoff point is the point, where  $I_C$  is very small approximately zero and  $V_{CE}$  is maximum of  $V_{CC}$  so it's given by;

$$V_{CE}^{(cutoff)} = V_{CC}, \quad I_C = 0.$$

cutoff = open  
saturation = close
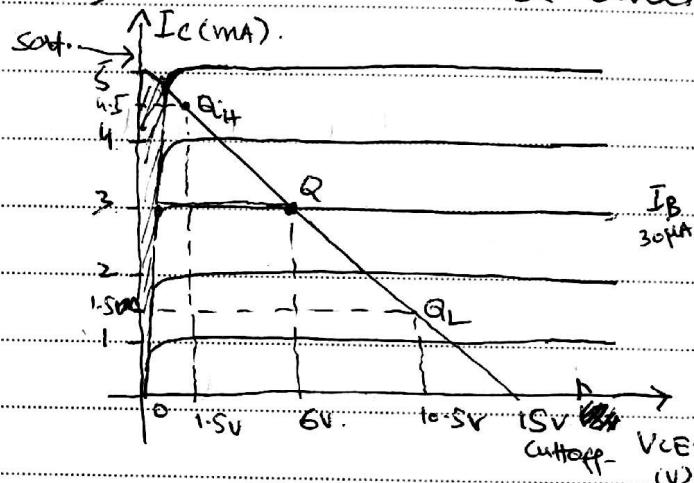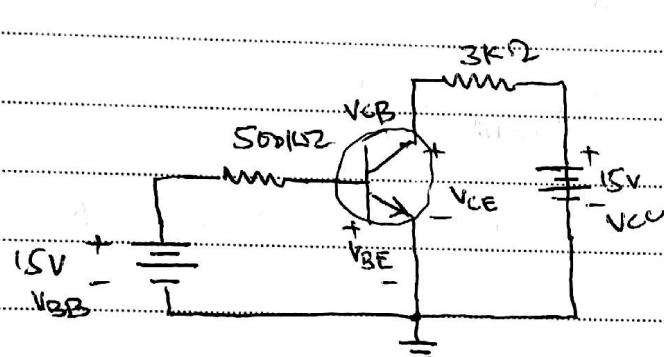
### 3 - The Operating Point.

The operating point or Q-point gives the operating coordinates of  $I_C$  (Collector current) and  $V_{CE}$  (Collector Emitter voltage) on the Load-line.



The operating point is plotted as:

Using Formulas we get the Transistor curve, Load line and then the Q-point.

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

$$I_C = \beta_{dc} I_B$$

$$V_{CE} = V_{CC} - I_C R_C$$

For Transistor curve.

For ideal Transistor :  $V_{BE} = 0$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{V_{BB}}{R_B} = \frac{15}{500k\Omega} = 30 \mu A$$

suppose.

$$I_C = \beta I_B = (100)(30 \mu A) = 3 \text{ mA.} \quad \beta_{dc} = 100$$

## For Load Line

Saturation point :  $I_C = \frac{V_{CC}}{R_C} = \frac{15}{3k\Omega} = 5mA.$   
 $I_C = 5mA, V_{CE} = 0$

Cutoff point :  $V_{CE} = V_{CC}$   
 $V_{CE} = 15V \quad \& \quad I_C = 0mA.$

## For Q-point

Here  $I_C = 3mA.$

$$\begin{aligned} \text{whereas ; } V_{CE} &= V_{CC} - I_C R_C \\ &= 15 - (3mA)(3k\Omega) \\ &= 15 - 9 \end{aligned}$$

$$V_{CE} = 6 \text{ Volts.}$$

$$\begin{aligned} I_C &= 3mA. \\ V_{CE} &= 6 \text{ Volts.} \end{aligned}$$


Drawing these points of  $I_C$  and  $V_{CE}$  gives the Q-point.

For variations in Beta value. ( $50 - 150$ )

For Low Q-point :  $I_C = B_{DC}(I_B)$

$$= 50(30\mu A) = 1.5mA.$$
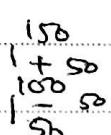
$$V_{CE} = 15V - (1.5mA)(3k\Omega) = 10.5V.$$



For High Q-point :  $I_C = B_{DC}(I_B)$

$$= 150(30\mu A) = 4.5mA.$$

$$V_{CE} = 15 - (4.5mA)(3k\Omega) = 1.5V.$$

## ► JFETs (Basics) : FETs >

FET stands for field Effect Transistor, which is a unipolar device, because it operates on the single type of charge carrier.


FET has two types

- (i) JFETs ( Junction Field Effect Transistor )
- (ii) MOSFETs ( Metal oxide semiconductor Field Effect Transistors ).

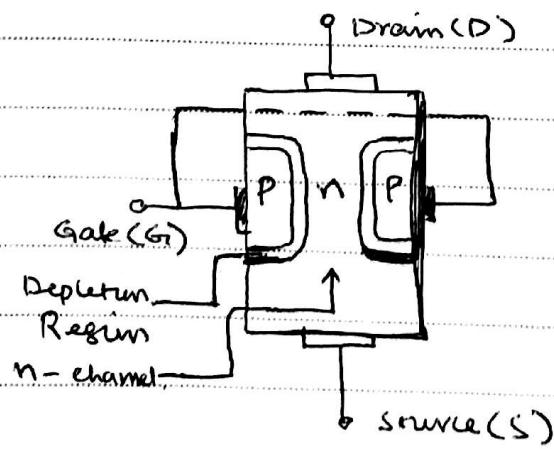
### 1- JFETs

JFETs (Junction Field Effect Transistor) is a type of FET that operates in a reverse bias condition of the pn-junction. JFETs has two main types n-channel JFETs & P-channel JFETs.

n-channel JFETs is formed by diffusing two P-type regions in the n-type material. The upper end is the Drain, lower end is the Source and the two P-regions are connected to the Gate.



(a) n-channel JFET

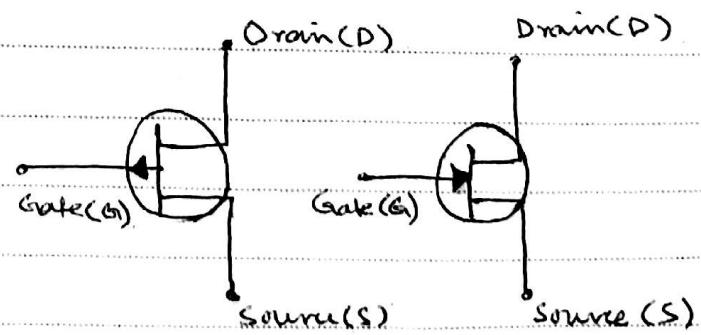

(b)- P-channel


(b)- (symbols.)



Visit [tshahab.blogspot.com](http://tshahab.blogspot.com) for more.

Dated:

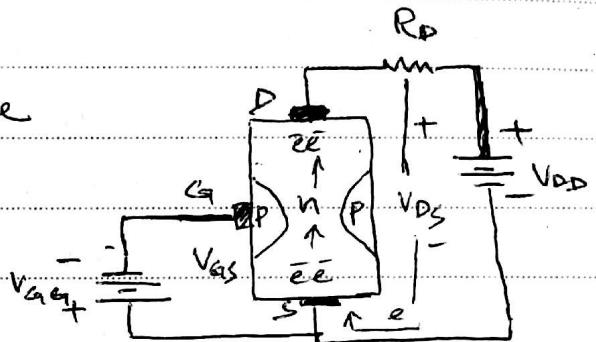JFET is operated with the Gate-Source pn-junction reverse bias. So  $V_{GS}$  set the reverse bias - voltage where as  $V_D$  is the drain voltage.



The electrons enter the source cross the p-n-junction and enter into drain, terminating at the V<sub>DD</sub> (+ve terminal). Through gate to source voltage ( $V_{GS}$ ) the width of the channel could be controlled thus controlling the Drain current ( $I_D$ ).

## 2- Drain Curves (JFET):



- The Drain curve is between the Drain Source Voltage ( $V_{DS}$ ) and drain current ( $I_D$ ) for the shorted Gate source voltage ( $V_{GS} = 0V$ ).

- For ohmic Region

JFETs behaves

as ohmic-resistance,

For Active-region drain

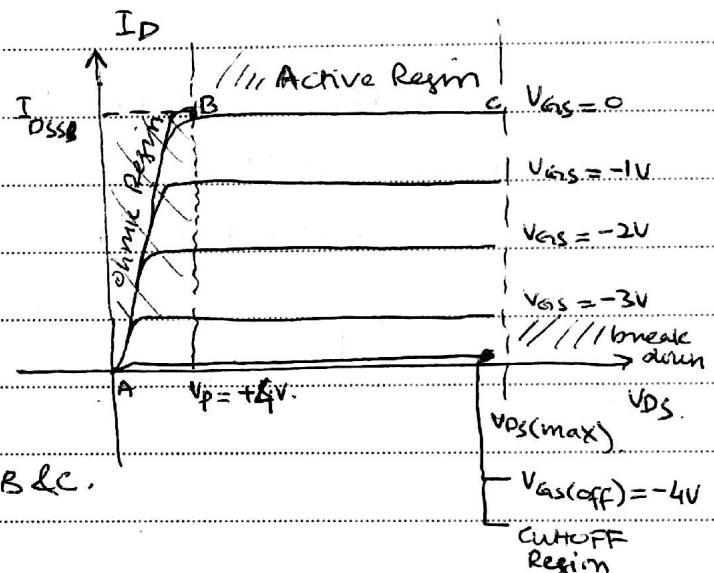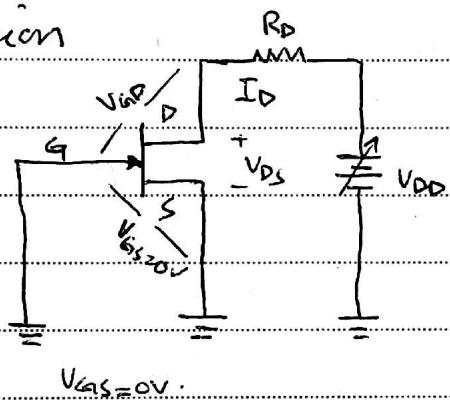

curremt remains constant between B & C.

- Pinch-OFF voltage : ( $v_p$ ) :

For  $V_{GS} = 0V$ , the value of  $V_{DS}$  for which there is a constant value of drain current ( $I_D$ ) is called Pinch-OFF voltage ( $v_p$ ). It's called as drain to source current with shorted Gate ( $I_{DSS}$ ).

For pinch OFF voltage condition is;

$V_{GS} = 0V$ ,  $I_D = I_{DSS}$  and  $V_{DS} = V_p$ . (minimum value of  $V_{DS}$ )

Cutoff Voltage : ( $V_{GS(OFF)}$ ) :

For  $V_{GS} = -v_p$ , the value of  $V_{DS}$  at which the drain current reaches its minimum value is called Cutoff Voltage ( $V_{GS(OFF)}$ ).


$V_{GS} = -v_p$ ,  $I_D = \min(0)$  and  $V_{DS} = \max$ .

### 3 - JFET - Transfer Characteristic Curve

The transfer characteristic curve is between the drain-current ( $I_D$ ) and Gate-Source Voltage ( $V_{GS}$ ) by using the values of Drain-Curve.

The transfer characteristic curve equations for JFET is given by:
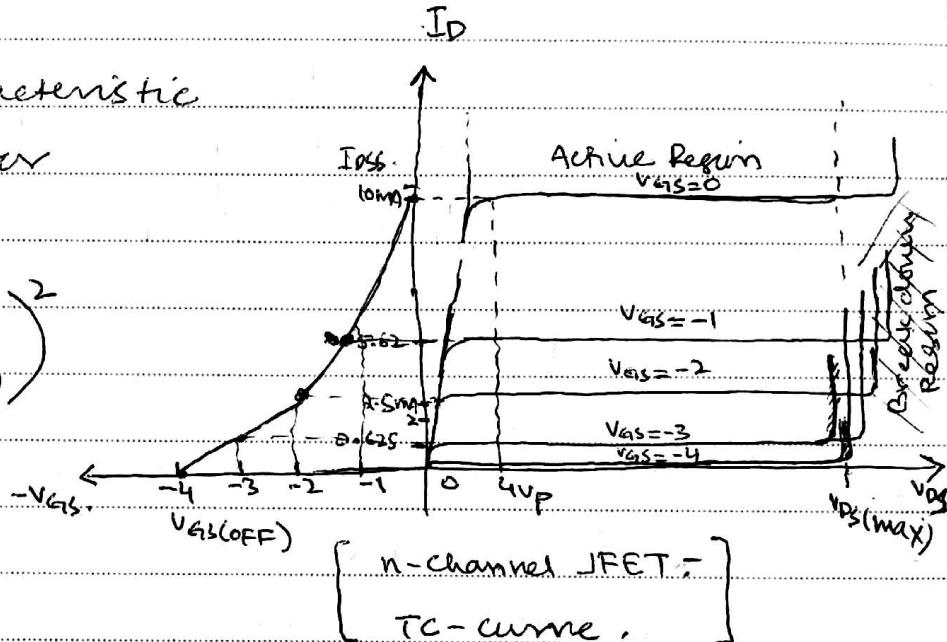
$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(OFF)}} \right)^2$$



The JFET- Transfer characteristic curve shows the operating limits of a JFET.

$$I_D = 0 \text{ when } V_{GS} = V_{GS(OFF)}$$

$$\& I_D = I_{DSS} \text{ when } V_{GS} = 0.$$

example : The JFET has a  $I_{DSS} = 9mA$  and  $V_{GS(OFF)} = -8V$ . Using these values find out  $I_D$ , for  $V_{GS} = 0V$ ,  $-1V$  and  $-4V$ .

Solution : For  $V_{GS} = 0V$ .

$$I_D = I_{DSS} = 9mA.$$

For  $V_{GS} = -1V$ .

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(OFF)}} \right)^2 = 6.89mA.$$

For  $V_{GS} = -4V$

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(OFF)}} \right)^2 = 2.25mA.$$

## 6- Comparison between BJT and FET


Bipolar Junction Transistor      Field Effect Transistor.

### BJT


- 1- BJT is a bipolar junction device i.e electrons & holes
- 2- BJT is a current controlled device ( $I_B$ )
- 3- BJT operates on the forward bias mode ( $V_{BE}$  - Emitter diode).
- 4- BJT are temperature sensitive devices
- 5- BJT are Large in size
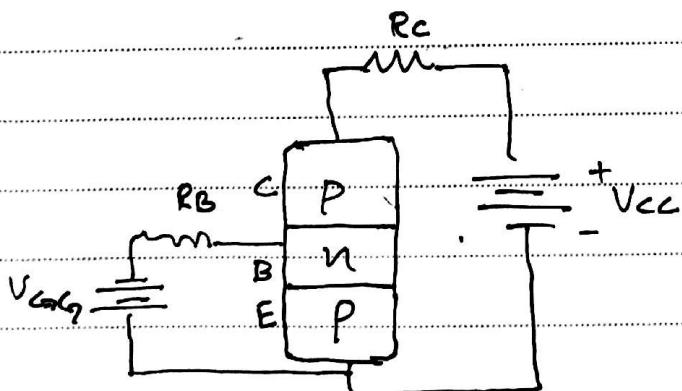
### FET

- 1- Field Effect Transistor is a unipolar device i.e n-channel or p-channel JFET.
- 2- FET is a voltage controlled device, ( $V_{GS}$ )
- 3- FET Operates on the reverse bias voltage ( $V_{GS} \Theta$ )
- 4- FET are temperature stable devices
- 5- FET are Smaller in size.



npn - BJT.

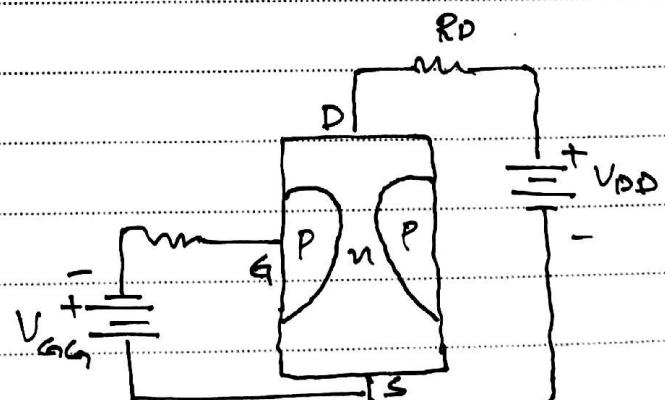

n - channel JFET.

## ► MOSFETS


MOSFETs is another type of FET, it stands for Metal-Oxide Semiconductor Field Effect Transistor. It differ from JFET in the structure that its Gate is isolated from the channel. Its also known as Insulated-Gate FET (IGFET).

### Types of MOSFET

- (i) - D-MOSFET. (Depletion)
- (ii) E-MOSFET (Enhancement)

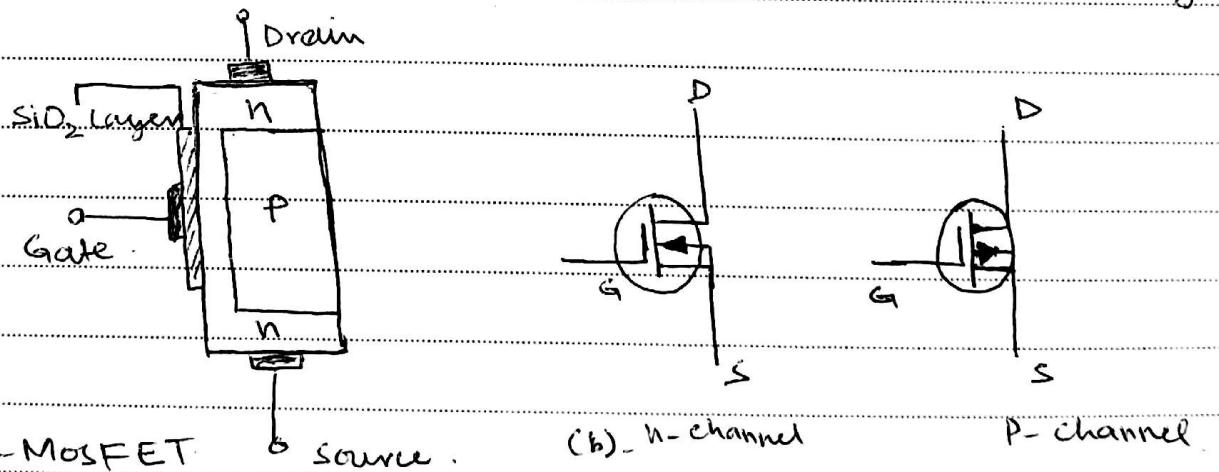
#### 1- D-MOSFET : (Depletion-Mode) >

D-MOSFET contains the n-region (narrow-channel) diffused into the substrate of p-region. Drain and Source are connected with n-region whereas Gate is insulated from the channel with  $\text{SiO}_2$  Layer.



In the D-MOSFET, the Gate-voltage is  $\ominus$ ve, whereas when the supply voltage  $V_{DD}$  forces free electrons, it flows from the source and then through the narrow channel towards the drain. Here gate just act as one plate of capacitor, channel as other plate of capacitor whereas  $\text{SiO}_2$ -layer is dielectric.

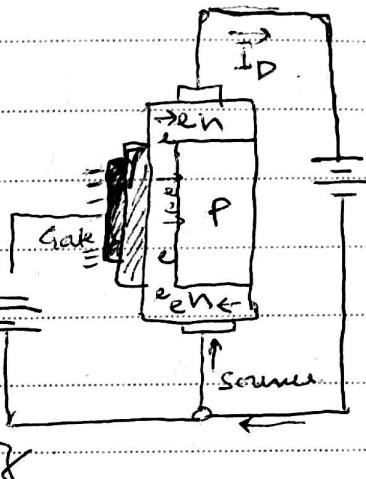
with the  $\ominus$ ve voltage on the Gate repels the conduction electrons from the channel, depleting n-channel from electrons, hence increasing  $\ominus$ ve voltage decreases the conductivity  $v_{sd}$  of the channel, whereas  $+$ ve voltage increases the channel conductivity.


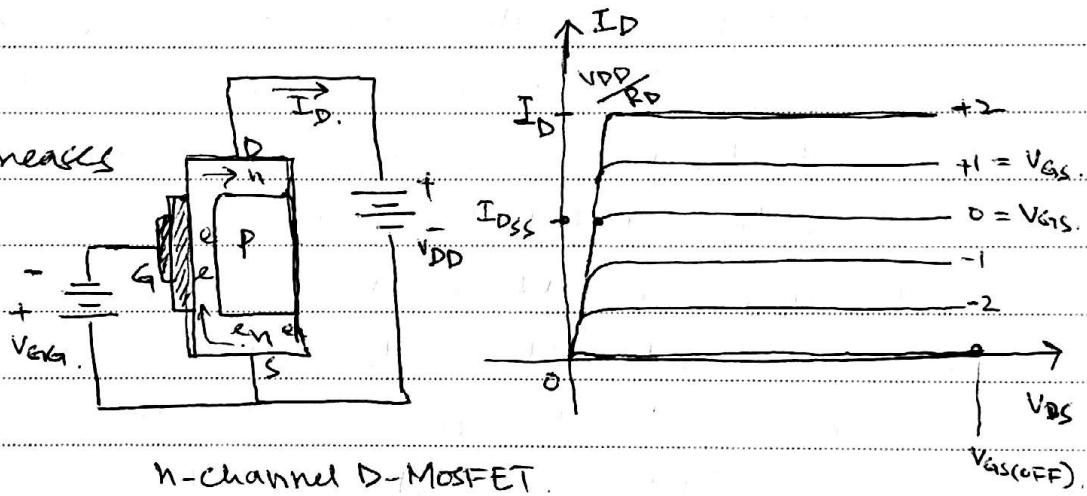
## 2. Drain Curves (D-MOSFET)

The Drain curve of n-channel D-MOSFET is similar to the JFET, and in between the Drain current ( $I_D$ ) and Drain source voltage ( $V_{DS}$ ). The only difference is that D-MOSFET is also operated in the  $\oplus V_{GS}$  voltage.

The Drain current ( $I_D$ ) decreases as the  $V_{GS}$  gets  $\ominus$ ve and  $I_D$  increases with the  $\oplus V_{GS}$ .



$I_{DSS}$  is the Drain current with shorted Gate, and is achieved when  $V_{GS}=0$ . Here  $I_{DSS}$  is no longer a maximum drain current.


$V_{GS(OFF)}$  is the cutoff point and is achieved when drain current is zero.

- Negative  $V_{GS}$  = Depletion-mode
- Positive  $V_{GS}$  = Enhancement-mode.
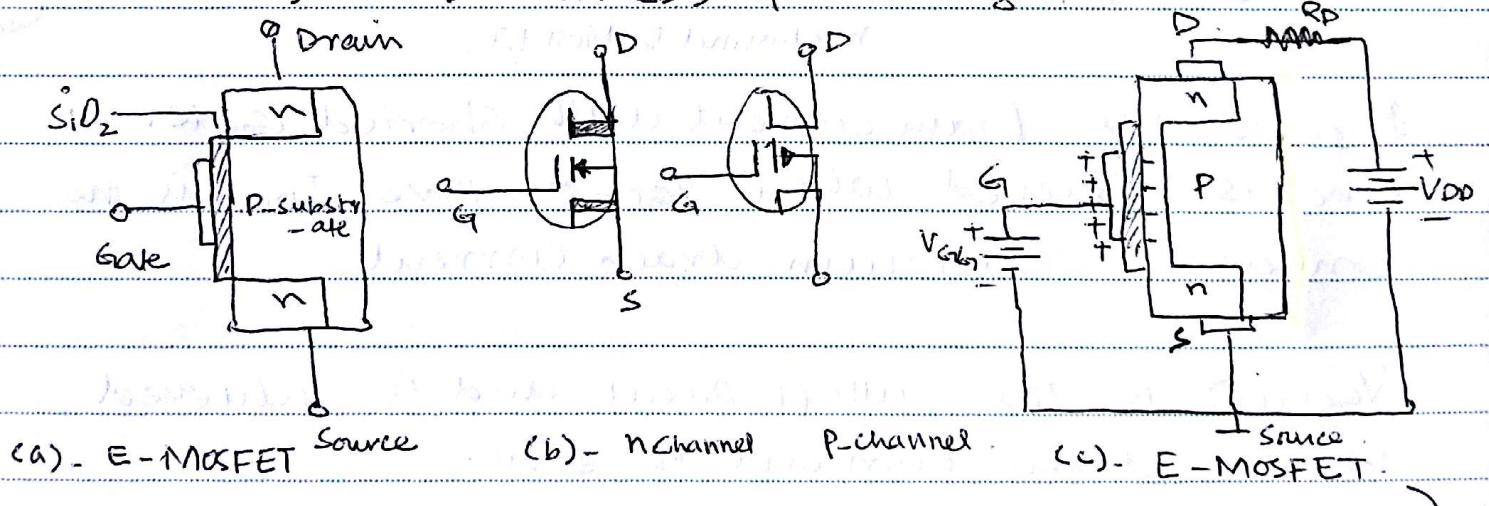
### 3- Enhancement Mode MOSFET (E-MOSFET)


Enhancement Mode MOSFET is formed, such that the P-substrate extends towards the  $\text{SiO}_2$  layer, and there is no n-channel.

E-MOSFET operates with the +ve gate source voltage ( $V_{GS}$ ). The positive gate (G) attracts the free-electrons into P-region, that (e), combines with holes, until the holes with the  $\text{SiO}_2$  layer fills up, resulting in a thin layer same as n-type material so the electrons flow from Source (S) to Drain (D) producing drain-current.



The Drain curve for E-MOSFET is for positive  $V_{GS}$  values.

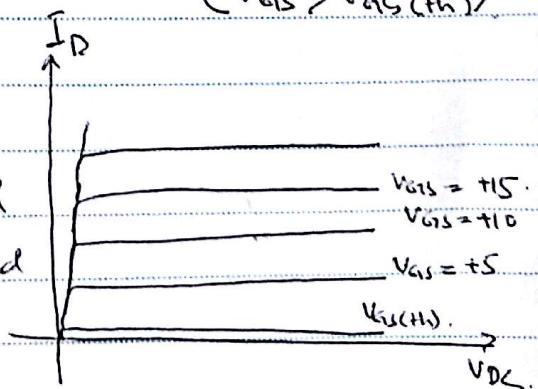The minimum  $V_{GS}$  that is required for the thin n-type layer is called threshold voltage ( $V_{GS(\text{th})}$ ).



## Reference Material:

- ① Principles of Electronics by VK Mehta.
- ② Electronic Principles by Albert Malvino  
(seventh Edition)

