

Note: Objective part is compulsory. Attempt any three questions from subjective part.

Objective Part (Compulsory)

Q.1. Write short answers of the following in 2-3 lines each on your answer sheet. (2*12)

- i. What are literals?
- ii. Write dual of $0 \cdot 1 = 1 \cdot 0 = 0$
- iii. Define null element theorem
- iv. What are decoders?
- v. What are priority circuits?
- vi. What are arithmetic circuits?
- vii. What is a propagation delay?
- viii. What is minimum number of bits that can be added using a full adder?
- ix. What are synchronous sequential circuits?
- x. A flip-flop copies input to output on which edge of the clock?
- xi. A divide-by-N counter has how many outputs?
- xii. What is a synchronizer?

Subjective Part (3*12)

Q.2. Simplify the following Boolean equations using Boolean theorems. Check for correctness using a truth table or K-map.


$$Y = \overline{A} \overline{B} \overline{C} \overline{D} + \overline{A} B \overline{C} \overline{D} + \overline{A} B C \overline{D} + \overline{A} B C D + \overline{A} \overline{B} C D + \overline{A} \overline{B} \overline{C} D + \overline{A} \overline{B} \overline{C} \overline{D}$$

Q.3. Draw a 4:1 multiplexer with minimum number of gates.

Q.4. Following table shows the truth table for a Boolean function Y. Using De Morgan's Theorem, derive the product-of-sums canonical form of Y from the sum-of-products form of complement of Y.

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

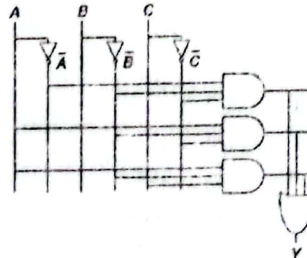Q.5. Given the following logic circuit, draw an equivalent logic circuit with max-terms.



Q.6. Find the propagation delay and contamination delay of the circuit shown in the following circuit. According to his data book, each gate has a propagation delay of 80 picoseconds (ps) and a contamination delay of 50 ps.

