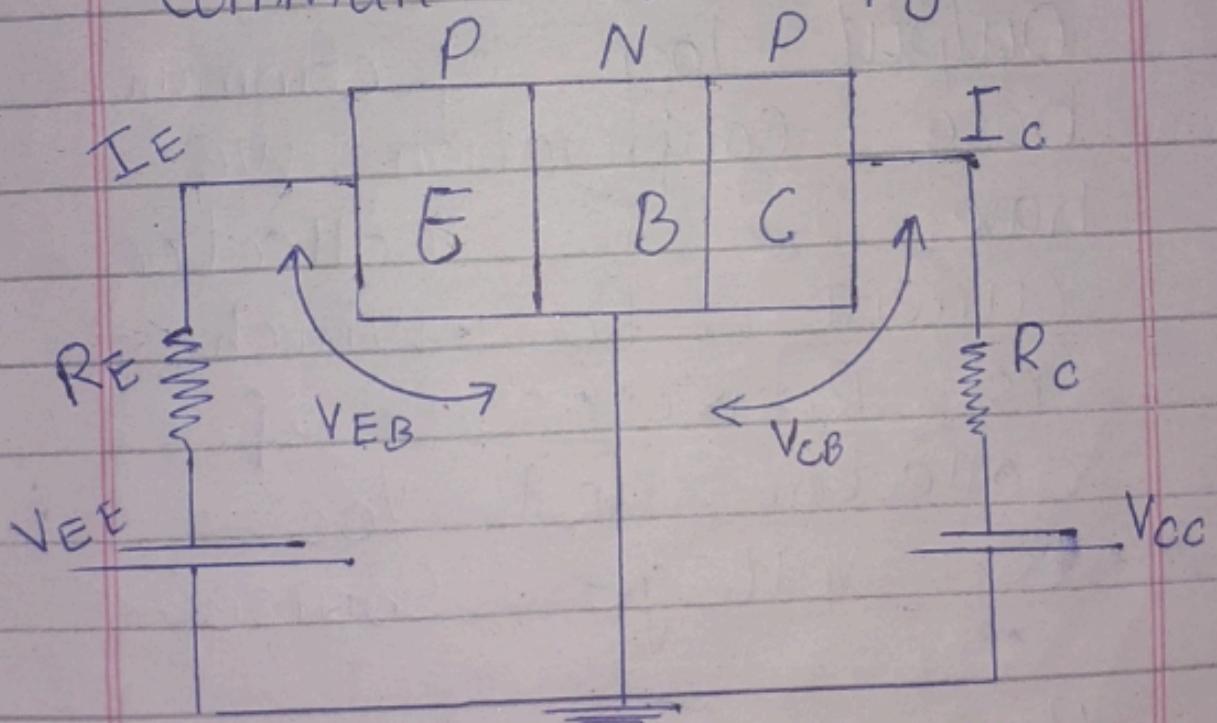


Imp
V/IQ

Common Base Configuration

The configuration of transistor in which base terminal are common between emitter and collector is known as Common base configuration.



Input:-

In Input loop of common base Configuration we have ~~Transistor is~~ is current

Resistance of emmitter.

$$V_{EE} = I_E R_E + V_{EB}$$

$$I_E = \frac{V_{EE} - V_{EB}}{R_E}$$

Output loop.

In

Output loop of common base Configuration we have I_c is collector current , R_C which is Resistance of collector and V_{CC} is voltage source.


Using ohm's law

$$V_{CC} = I_c R_C + V_{CB}$$

$$I_c = \frac{V_{CC} - V_{CB}}{R_C}$$

Input characteristics:

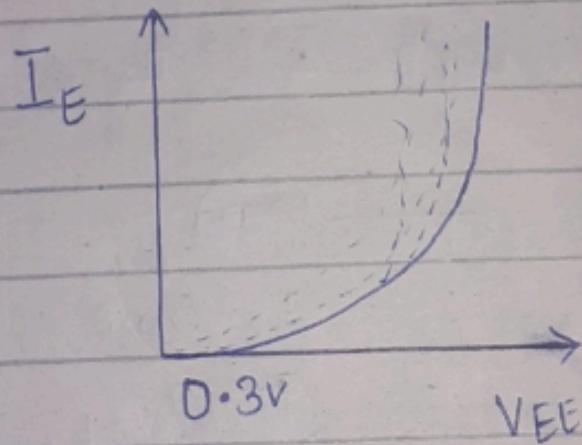
The graph between I_E and V_{EE} of common base Configuration is known as Input characteristics.



We used germinum voltage which is $0.3V$

Output characteristics

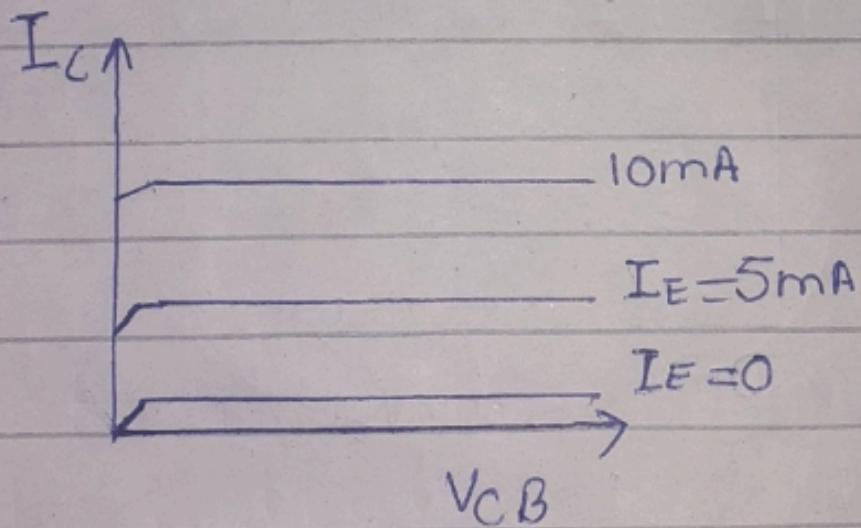The graph between I_C and V_{CB} in common base configuration is known as output characteristics.



Input Resistance

The opposition force offered to input signal in Input loop.

$$R_{in} = \left(\frac{V_{EB}}{I_E} \right)_{V_{BC}}$$

Input Conductance

The Reciprocal of Input Resistance is known as Input conductance.

$\Rightarrow g_t$ is denoted by G_{in}

$$G_{in} = \frac{1}{R_{in}}$$

$$G_{in} = \frac{1}{\left(\frac{V_{EB}}{I_E} \right)_{V_{BC}}}$$

Output Resistance

The opposition offered to ~~input~~ signal in Output loop is known Out put Resistance

$$R_{out} = \left(\frac{V_{CB}}{I_c} \right)_{IE=0}$$

Output Conductance

Resist The reciprocal of output Resistance is known as Output Conductance.


→ Denoted by G_{out}

$$G_{out} = \frac{1}{R_{out}}$$

$$G_{out} = \frac{1}{\left(\frac{V_{CB}}{I_C} \right)_{IE}}$$

Current gain characteristics:-

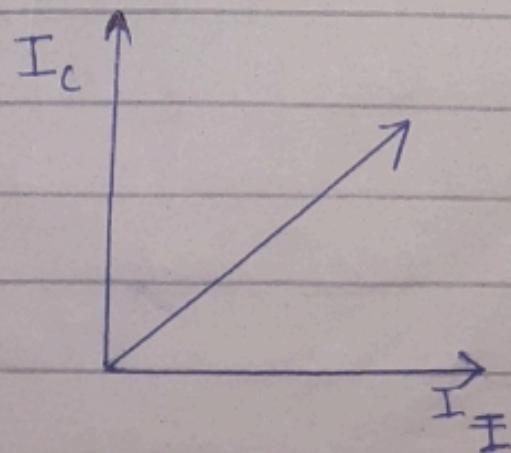The graph between I_E and I_C at constant V_{CB} is called current gain characteristics, and graph between I_C and I_E gives straight line.




\Rightarrow obey the Ohm's Law

\Rightarrow Represent by α
and

$$\alpha = \left(\frac{I_C}{I_E} \right) V_{CB}$$

Common Emitter Configuration

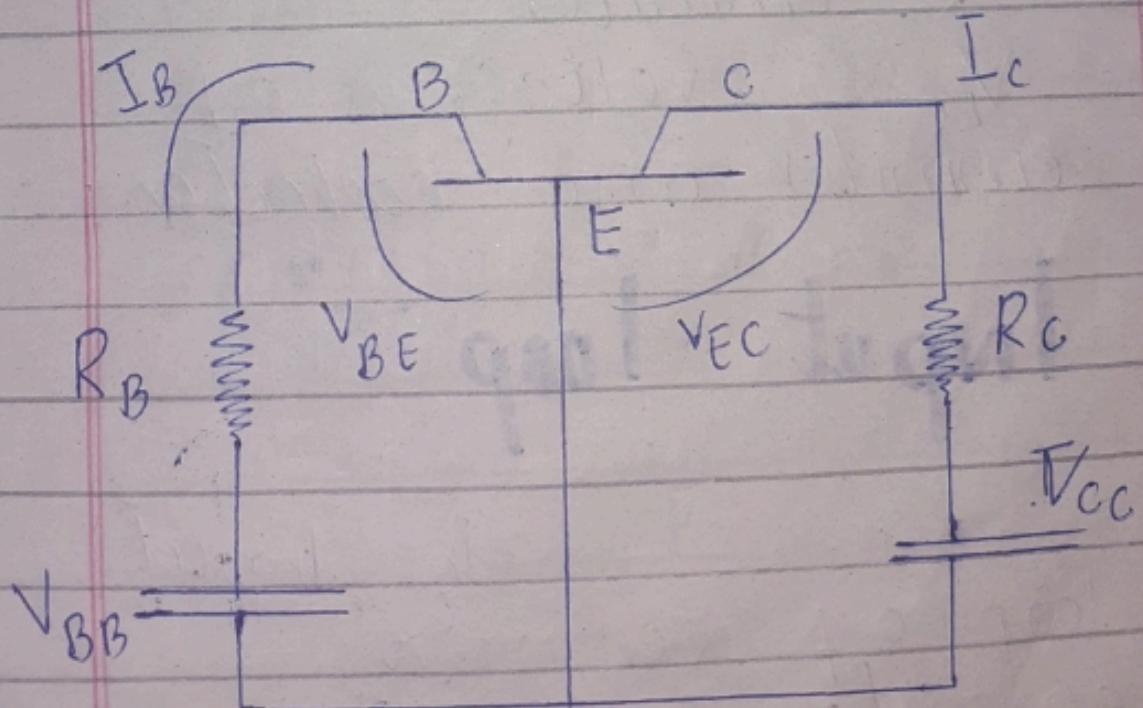The Configuration of Transistor in which emitter terminal is common between Base and collector is known as common emitter configuration.



$I_B \rightarrow$ current of Base
 $R_B \Rightarrow$ Resistance of Base

$V_{BB} \Rightarrow$ external voltage of Base

$I_C \Rightarrow$ current of collector

$R_C \Rightarrow$ Resistance of collector.

$V_{CC} \Rightarrow$ external voltage of collector

$V_{BE} \Rightarrow$ voltage of Base & emmiter

$V_{EC} \Rightarrow$ voltage of emmiter and collector.

Input loop

In Input loop of common emmiter configuration

We have I_B which is Base current

, R_B is Resistance of Base and V_{BE} which is a Input voltage

$$V_{BB} = I_B R_B + V_{BE}$$

$$V_{BB} - V_{BE} = I_B R_B$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

Output loop:-

In

Output loop of common emitter configuration we have I_c is

collector current,

R_C is Resistance of collector and V_{CC} is output voltage.


$$V_{CC} = I_c R_C + V_{EC}$$

$$V_{CC} - V_{EC} = I_c R_C$$

$$I_c = \frac{V_{CC} - V_{EC}}{R_C}$$


Input characteristics:-

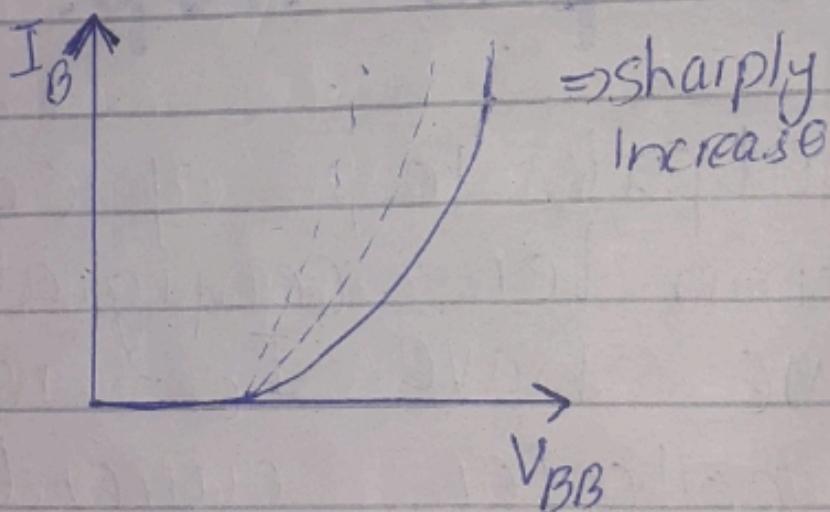The graph between I_B and V_{BB} in common emitter configuration is known as Input characteristics.



Output characteristics

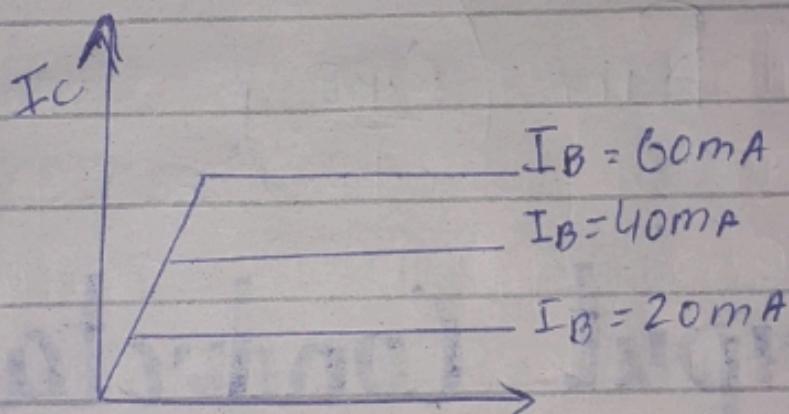The graph between I_C and V_{CE} in common emitter configuration is known as Output characteristics.



Input Resistance:-

The opposition force offered to input signal in input loop is known as Input Resistance.

$$R_{in} = \left(\frac{V_{BE}}{I_B} \right) V_{BC}$$

Input Conductance

The reciprocal of Input Resistance is known as Input conductance.

$$G_I = \frac{1}{R_{in}}$$

$$G_I = \frac{1}{\left(\frac{V_{BE}}{I_B} \right) V_{BC}}$$

$$G_{in} = \left(\frac{I_B}{V_{BE}} \right)_{V_{BC}}$$

Output Resistance :-

The opposition force offered to output signal in output loop is known as Output Resistance.

$$R_{out} = \left(\frac{V_{OC}}{I_C} \right)_{I_B}$$

Output Reconductance

The reciprocal of output Resistance in common emitter configuration is known as output conductance.

→ Denoted by G_f

$$G_I = \frac{1}{R_{out}}$$

$$G_I = \frac{1}{\left(\frac{V_{cc}}{I_c} - \frac{I_c}{I_B} \right)} \quad \left(\frac{I_c}{V_{cc}} \right)_{IB}$$

choice of Wavelength