

Date: _____

"LECTURE"


M T W T F S

⇒ APPLIED PHYSICS

Q. ZERO REFERENCE LEVEL = .

In order to avoid errors in different measurements on voltage of an electronic circuit. It is essential to Select same common points as known as zero reference level.

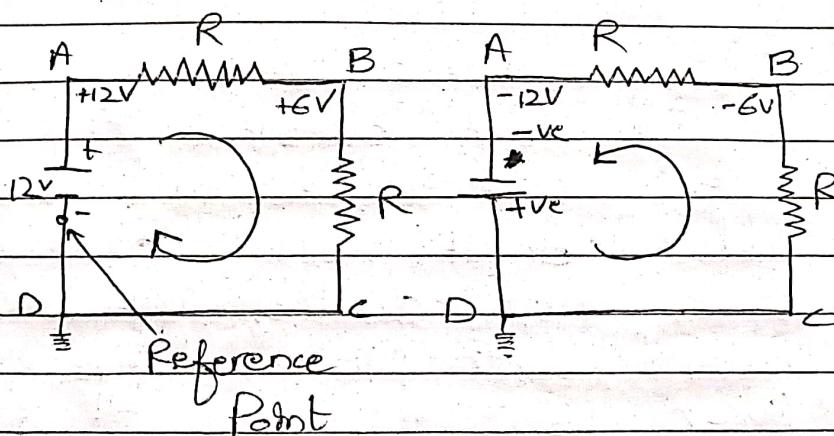The point to be selected as reference point can be any point in the circuit and need not necessarily be at zero volt.



$$\text{P.E} = \text{charge} + \text{P.D}$$


⇒ Reference point is compulsory to measure Voltage.

⇒ DC is a constant magnitude.

⇒ DC is much powerful than max AC.


Date: _____

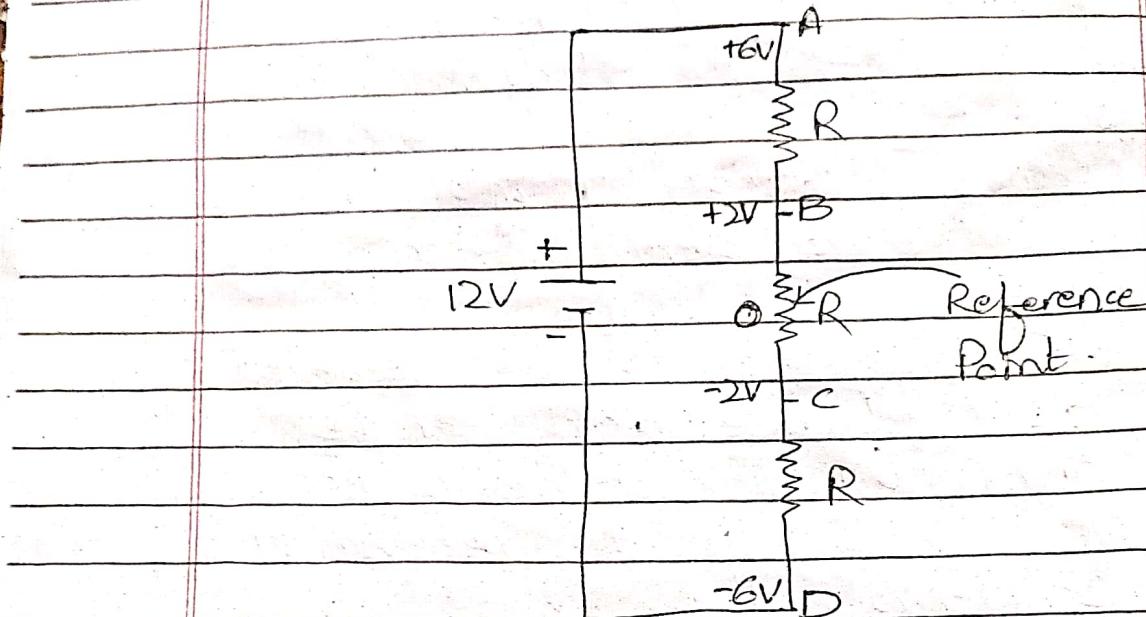- ⇒ Blood is a electrolyte.
- ⇒ Current flows due to potential difference.




Q = CHASSIS GROUND:

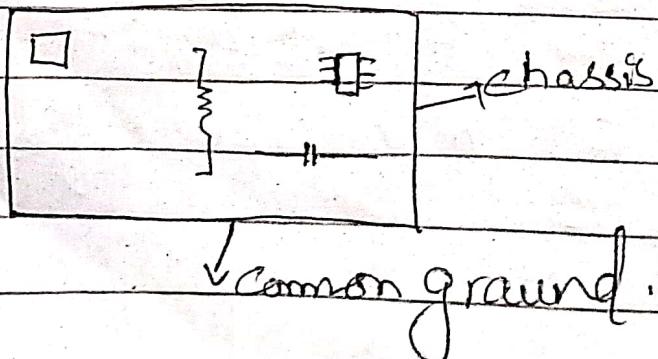Generally electronic component are mounted on conducting metal sheet called chassis or a non conducting Plastic board with printed wire. When using chassis, it is common practice to treat the body of chassis itself as common ground.



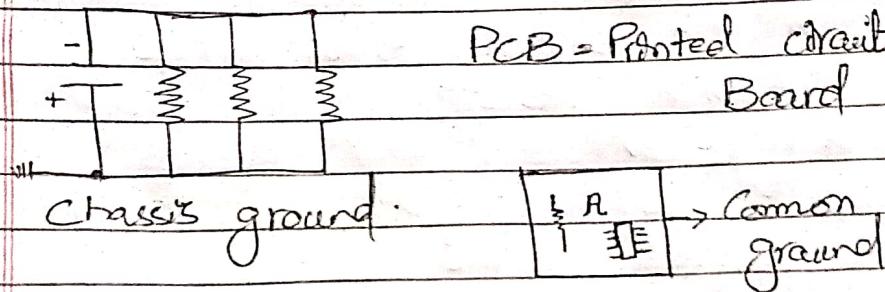- i) Conducting metal sheet.
- ii) Non-conducting plastic board.



- ⇒ The conducting metal act as a chassis ground.
- ⇒ If path is not close the current flows not occur.
- ⇒ The boundary of plastic board work as Chassis ground.
- ⇒ The energy charge work as a energy carrier from the source of energy is called Potential difference or Voltage.
- ⇒ The device which can convert to electric energy is called source of energy.
- ⇒ The work of source is to give charge a direction.

Date:

Q. OHM'S LAW

In circuits energised by DC voltage sources, there exists a definite relationship between the current (I) that flows through resistance (R) and voltage (V) applied across the resistance. This relationship is called ohm's law.

$$I = \frac{V}{R}$$

Here,

 I = current V = Voltage R = Resistance

Current here is directly proportional to voltage and inversely proportional to resistance.

Formula Variations for Ohm's Law

for current -

$$I = V/R$$

for Voltage -


$$V = IR$$

for resistance -


$$R = \frac{V}{I}$$

Date: _____

M T W T F S

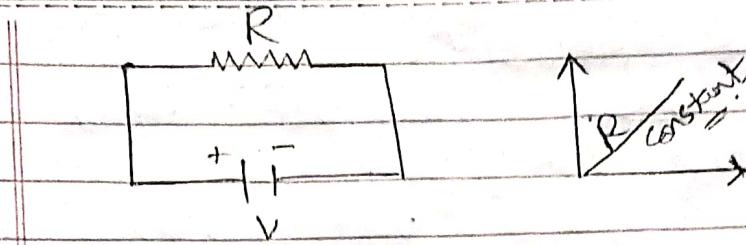

Q. GRAPHICAL REPRESENTATION OF OHM'S LAW

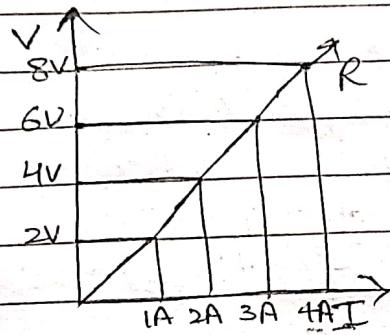

for resistance,

$$R = \frac{V}{I} \quad , V = IR$$

$$R = ? \rightarrow V = 4V \quad , I = 2A$$

$$R = \frac{V}{I} = \frac{4V}{2A} = 2\Omega$$

\Rightarrow Material that obey ohm's law (filament) are called ohmic material.

\Rightarrow Materials that don't obey ohm's law are called non-ohmic material: LED Bulb Semiconductor

Date: _____

(Q.) LINEAR RESISTOR

A resistor whose value remain constant, it does not depend upon applied voltage. The V-I characteristic of such resistors is a straight line

$$V \propto I$$

(Q.) NON-LINEAR RESISTOR

Resistors in which V and I are not directly proportional to each other. If applied voltage is doubled, the resultant current, is not exactly doubled of its previous value. Such resistors are called Non-linear.

(Q.) WORK & POWER

\Rightarrow WORK =

Ability to do something is called work.

\Rightarrow Power =

Rate of doing work is called power.

$$P = \frac{W}{T} = \frac{E(\text{energy})}{T} = \frac{VI}{T} = VI$$

In term of Voltage & current.
unit = watt.

Date: _____

M T W T F S

So,

we have

$$\boxed{P=VI}$$

and we know ($V=IR$) in ohms

Law:

So,

$$P = (IR) I$$

$$\boxed{P = I^2 R} \text{ (Power loss)}$$

for resistor in series.

And,

$$I = \frac{V}{R} \quad \therefore I = \frac{V}{R}$$

$$P = \left(\frac{V}{R}\right)^2 \cdot R \Rightarrow P = I^2 R$$

$$P = \frac{V^2}{R} \cdot R$$

$$\boxed{P = \frac{V^2}{R}}$$

for resistors in Parallel.

Lecture

=> PHYSICS.

SHORT CIRCUIT


It is a close circuit whose resistance is zero. It is almost negligible.

OPEN CIRCUIT


It is an off circuit whose resistance is infinite.

=> Resistance of gap is infinite.

"Ref. Book page N10-17"

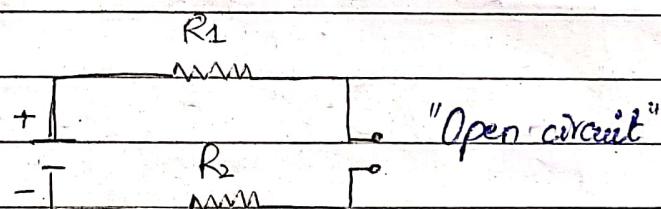

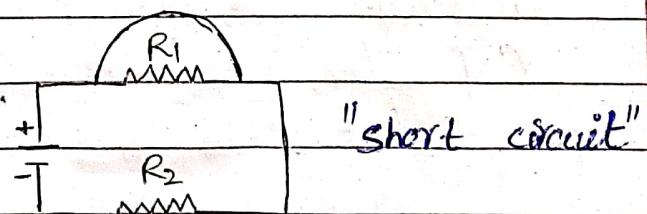=> In open circuit voltages appear across end point or open points.




=> In short circuit current passes through the path having low resistance.

SHORT CIRCUIT AND OPEN CIRCUIT IN PARALLEL


OPEN CIRCUIT IN PARALLEL

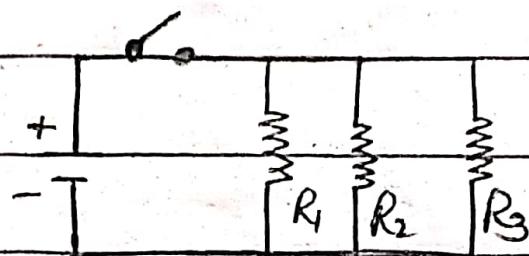We use open circuit in parallel in order to save the connected resistances from breakage or disorder.



SHORT CIRCUIT IN PARALLEL

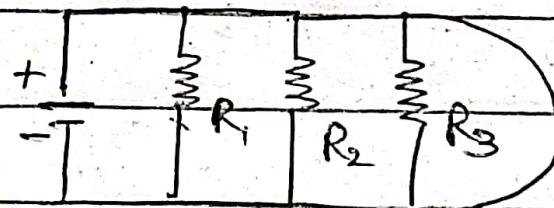
We use short circuit for parallel to provide easy path for the flow of current in parallel.



\Rightarrow CAPACITANCE -

The ability of capacitor to store electric charge is called capacitance.

Its unit is farad.

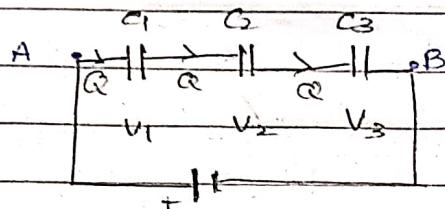 \Rightarrow CAPACITOR IN SERIES -

In series charge remains the same and voltages split.

$$Q = CV$$

and

$$V = Q/C$$

and we know,

$$V = V_1 + V_2 + V_3$$

$$\frac{Q}{C_{eq}} = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3} \quad \therefore V = Q/C$$

$$\frac{Q}{C_{eq}} = Q \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)$$


$\frac{1}{C_{eq}}$	$\frac{1}{C_1}$	$\frac{1}{C_2}$	$\frac{1}{C_3}$
--------------------	-----------------	-----------------	-----------------

If we have capacitance in series we add them by reciprocal:

Date: _____

 \Rightarrow CAPACITOR IN PARALLEL

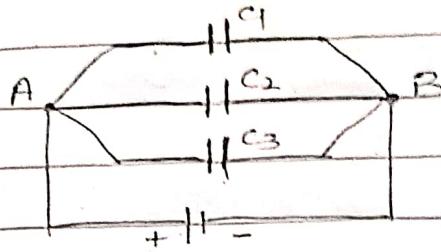IN Parallel voltage remains same and charge splits.



$$Q = CV$$


So

$$Q = Q_1 + Q_2 + Q_3$$

$$C_{eq} V = C_1 V + C_2 V + C_3 V$$

$$C_{eq} V = V (C_1 + C_2 + C_3)$$

$$C_{eq} = C_1 + C_2 + C_3$$

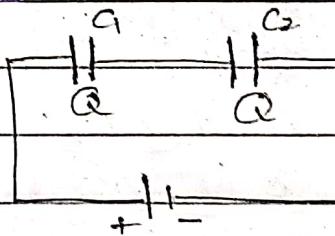 \Rightarrow Two CAPACITORS IN SERIES =As we connect two capacitor
in series

we get

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} \quad (\text{Applying } \frac{1}{R} \text{ formula})$$

$$= \frac{C_2 + C_1}{C_1 C_2}$$

Taking reciprocal =

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

=> finding Voltages in Series for two capacitors

$$V_1 = ?$$

$$Q = C_1 V_1$$

$$\Rightarrow V_1 = \frac{Q}{C_1} = \frac{V_{\text{eq}}}{C_1} \therefore Q = V_{\text{eq}}$$

$$= \frac{V}{C_1} \times \frac{C_1 C_2}{C_1 + C_2} \therefore \text{formula of } (C_{\text{eq}})$$

$$V_1 = \frac{V C_2}{C_1 + C_2}$$

=> finding Capacitance in series for two capacitors =

$$Q_1 = V C_1$$

$$= \frac{Q}{C_{\text{eq}}} \times C_1 \therefore V = \frac{Q}{C_{\text{eq}}}$$

$$= \frac{Q}{C_1 + C_2} \times C_1 \therefore C_{\text{eq}} = C_1 + C_2$$

$$Q_1 = Q \frac{C_1}{C_1 + C_2}$$


"LECTURE"

RHEOSTATE AND POTENTIOMETER.

A circuit used to give continuously varying resistance and varying potential.

Describe a circuit which will give continuously varying potential.

I/P.

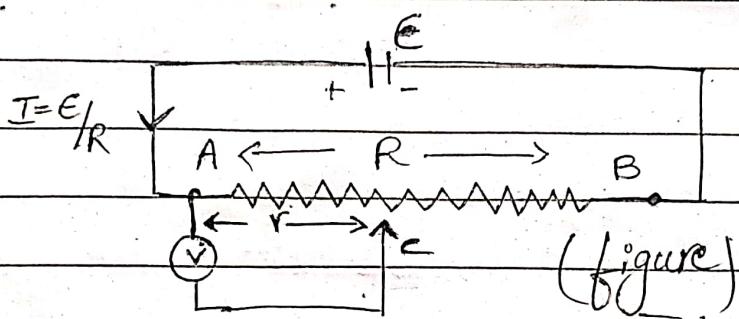

(figure)

C is a sliding terminal used to vary value of resistance/potential.

If sliding terminal is set to
(A) current will pass at maximum. ($A \rightarrow C$) .

If sliding terminal is set to half of the slide current will start passing at half of given or attached resistance.

If sliding terminal is set to move at Point B the resistance will be maximum and we will also change potential ($A \rightarrow B$).

We say that =

at A /

O.

Slide

At B

E.

$$\gamma = 0$$

$$\gamma = R$$

RHEOSTAT = (fixed, variable, Potential divider)

A device that uses a sliding resistance that is used to control resistance , current or potential of circuit is called "Rheostat".

POTENTIOMETER -

A variable resistance with a third adjustable terminal . The potential at third terminal can be adjusted to give any fraction of potential across the end of the resistor.

To equal the potential difference
we move sliding terminal
"A" towards "B" to equal potential
difference between small battery
attached to galvanometer and
circuit.

After,

$$V_{AC} = E_x$$

So,

$$E_x > V_{AC}$$

$$E_x = V_{AC} = I/R$$

$$E_x = I_R$$

$$E_x = E_{x1} \cdot \frac{R}{R} \quad \therefore I = \frac{E}{R}$$

$E_x = \frac{E_{x1} \cdot l}{l}$	Measure battery potential
----------------------------------	------------------------------

$F_1 = \frac{E_{x1} \cdot l}{l}$

$F_2 = \frac{E_{x2} \cdot l^2}{l}$

So,

$$\underline{E_1} = \underline{\frac{E_{x1} \cdot l}{l}}$$

$$\underline{E_2} = \underline{\frac{E_{x2} \cdot l^2}{l}}$$

$\underline{E_1} = \underline{\frac{l}{l^2}}$	Measure potential difference b/w two batteries.
---	---

Date: _____

M T W T F S

If Ratio is 1 -
Put,

$$\frac{E_1}{E_2} = 1$$

$$E_2$$

$$[E_1 = E_2]$$

If ratio is 2 =
Put,

$$\frac{E_1}{E_2} = 2$$

$$E_2$$

$$[E_1 = 2E_2]$$

"LACTURE"MUTUAL INDUCTION:

The phenomena of changing current in a coil to produce e.m.f in another coil is called mutual induction.

"Bellini" (flux)-BACK EMF=

The EMF produced in secondary coil by mutual induction starts opposing the primary EMF is called Back EMF.

~~- Opposite to primary EMF~~

BACK EMF=

$$M = - \frac{ES}{\Delta I P / \Delta t}$$

$$\Rightarrow ES = - M \frac{\Delta I P}{\Delta t}$$

INDUCTION IN SERIES=

$$L = L_1 + L_2$$


INDUCTION IN PARALLEL=

$$\frac{1}{L} = \frac{1}{L_1} + \frac{1}{L_2}$$

$$\frac{1}{L} = \frac{L_1 + L_2}{L_1 L_2}$$

$$\Rightarrow L = \frac{L_1 L_2}{L_1 + L_2}$$

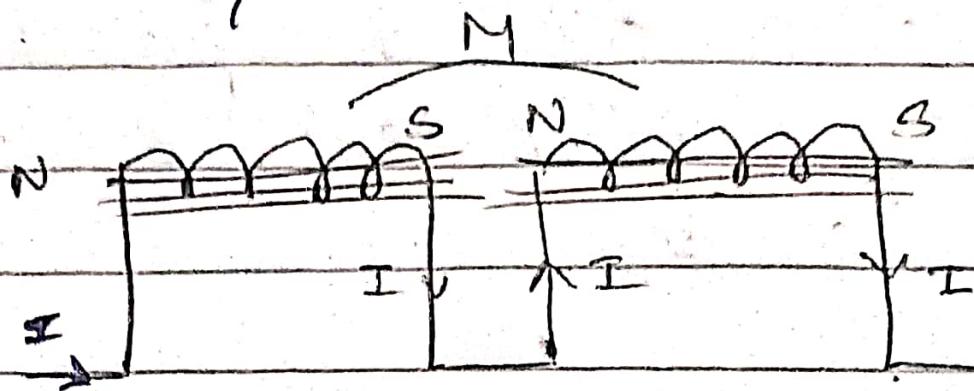SERIES Supporting
In series connection of induction coils support EMF of every coil ("South to north")



$$L_a = L_1 + L_2 + 2M$$

SERIES Opposing
In parallel connection of induction coils oppose EMF of every coil ("North to North")

In mutual induction coils are connected magnetically.

It has two resistance AC Resistance (X_L) and DC Resistance (R).

Reactance of capacitor = (X_C) (AC)

Reactance of capacitor decreases as frequency increases.
$$X_C \propto \frac{1}{f}$$

$$X_C \propto \frac{1}{C}$$

$$X_C \propto \frac{1}{f_C}$$

$$X_C = \frac{1}{2\pi f C} \therefore \boxed{X_C = \frac{1}{\omega C}}$$

Inductance of capacitor (X_L) (DC)

$$X_L \propto f$$

$$X_L \propto L$$

$$X_L \propto fL$$

$$X_L = 2\pi f L$$

$$\boxed{X_L = \omega L}$$

The combined of capacitor and resistor is called Impedance.

formula =

$$Z = \sqrt{X_L^2 + R^2}$$

Date: _____

\Rightarrow Phase Difference =

$$\tan \theta = \frac{X_L}{R}$$

$$\theta = \tan^{-1} \left(\frac{X_L}{R} \right)$$

\Rightarrow Quality factor =

$$\left| Q = \frac{X_L}{R} \right|$$

\Rightarrow Flux =

The total number of electric field lines passing a given area in a given time is called electric flux.

\Rightarrow ELECTROMAGNETIC INDUCTION =

The production of electromotive force across a conductor in changing magnetic field.

\Rightarrow CO-EFFICIENT OF COUPLING =

The fraction of magnetic flux produced in one coil that links with the other is called coefficient of coupling.

The magnetic flux is always produced by current in a coil.

It is represented by "K".

"LECTURE"

⇒ ENERGY SOURCES =

A potential difference devices are energy sources.

The devices that convert non-electrical energy into electrical energy are called energy sources.

EXAMPLES =

Cells & Batteries, Solar cells.

= TYPES OF SOURCES =


i) AC Sources.

ii) DC Sources.

AC CURRENT =

A current that changes its magnitude and direction continuously is called AC current.

SYMBOL =

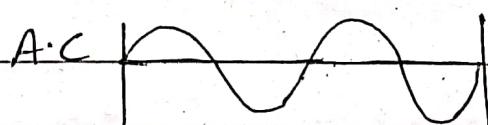

DC CURRENT =

Unidirectional current having constant magnitude is called DC current.

Date: _____

SYMBOL =

D.C



Q = VOLTAIC CELLS =

TYPES OF CELLS =

i) PRIMARY CELL =

A cell in which chemical reaction is not reversible or rechargeable (Clock cells)

ii) SECONDARY CELLS =

A cell in which chemical reaction is reversible and rechargeable (UPS Battery, Li-ion battery).

CHARACTERISTICS OF PRIMARY & SECONDARY CELLS =

REFERENCE ON

Book PAGE = 77.

⇒ BATTERY =

A combination of two or more cells is called battery.

Initial value of cell is 1.5V.

Initial value of battery is 3V.

⇒ DIFFERENT TYPES OF CELLS =

REFERENCE ON

Book PAGE = 77

Date: _____

M T W T F S

⇒ PHOTOVOLTAIC CELLS

A cell that convert light energy into electrical energy directly. It is also known as Solar Cell.

⇒ VOLTAIC CELLS

It is a combination of materials which produce direct current (dc) from its internal reactions.

Date: 02/03/23

M T W T F S

"Lecture"

=> LINE LOSS

Loss in a line Power
due to resistance is
known as line loss.

=> Power loss formula : " $P = I^2 R$ "

and we know,

$$I_s \propto \frac{1}{V_s} \quad (i)$$

=> as inverse variation we
increase voltages (i) by power
transformers on generating stations
to minimize losses caused
by resistance of ($I^2 R$).

=> Basically, power transformers are
used to carry power.

=> EDDY CURRENT:

Current produced in the
body of core by changing the
magnetic flux is called Eddy
current.

Date: _____

M T W T F S

Date: _____

=> To minimize eddy current losses we use laminated iron core instead of solid iron core in transformer.

=> Hysteresis loss =

The power loss that occurs due to magnetisation and de-magnetisation of core is called hysteresis loss.

=> We can improve efficiency of transformer by reducing eddy current & hysteresis losses in transformer.

=> Impedance of transformer can be found by formula

$$Z_2 = \sqrt{R'^2 + X_L'^2}$$

and

$$Z = \sqrt{R^2 + X_L^2}$$