

University of Sargodha

BS 2nd Term Examination 2019

Subject: Computer Science

Paper: Digital Logic Design (CMP-2210)

Time Allowed: 2:30 Hours

Maximum Marks: 80

Note: Objective part is compulsory. Attempt any three questions from subjective part.


Objective Part (Compulsory)

- Q.1.** Write short answers of the following in 2-3 lines each on your answer sheet. (16*2)
- Convert the given number $(144)_8$ into binary?
 - Use 10's complement to perform $M-N$ when $M=85320$ and $N=51360$
 - Write the following function into maxterms $F=\sum(2,4,5,6)$
 - State Duality principle?
 - Using postulates and theorems of Boolean algebra prove $x+xy=x$
 - Simplify the following Boolean function using k-map
 $F(A,B)=A'B'+AB'+AB$
 - Draw the Truth table of half subtractor and write the Boolean function for its Borrow and Difference?
 - What is the multiplexer?
 - Draw the logic circuit which performs addition between two input values?
 - Define Register and its type?
 - What is Karnaugh?
 - Obtain the 1's and 2's complement of the following binary function
 $0010001, 0111010, 010100, 1011101$
 - Draw the gate implementation of the following expression.
 $AB+A(B+C)+B(B+C)$
 - Prove that exclusive-OR is the complement of exclusive-NOR?
 - Expand the following Boolean functions into their canonical form:
 $f(A, B, C) = AB + A'C + AB'C$
 - What is 4-bit binary parallel adder?

Subjective Part (3*16)

- Q.2** Determine the base b in each of the following cases:
- $(361)_{10} = (551)_b$
 - $(982)_{10} = (1726)_b$

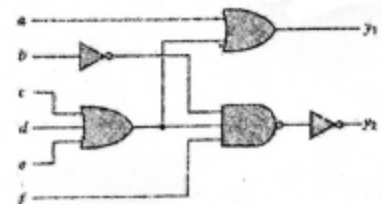- Q.3.** Write Boolean expressions and construct the truth tables describing the outputs of the circuits described by the logic diagram.



- Q.4.** Simplify the Boolean function
 $F(w, x, y, z) = \sum(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$. Find both SOP and POS expression.
- Q.5.** Draw circuit diagram of half adder and full adder. Draw truth table of half adder. Also write expression of half adder only. Show how a full adder can be converted to a full subtracter?
- Q.6.** What is Demultiplexer? Explain with 2 to 4 line Decoder with enable input and define its truth table and block diagram?