

# Past Papers

Binary	1's	2's
base 10	<del>decimal</del>	
Octal	4's	10's
	2's	3's
	4's	

## 2018

- ⇒ (ii) obtain 1's & 2's Complement  
of the following binary function

10110110

11010101

1's Complement

01001001

00101010

2's Complement

01001010

00101011

- ⇒ (iii) Represent the decimal No  
1122 in

(1) Excess -3

0100010010001000

(2) 84-2-1

0111011101100110

- ⇒ (iv) Simplify the function

$$(1) F(w, x, y, z) = \Sigma(0, 1, 3, 4, 8, 10, 14)$$

What is S-R latch? Draw logic diagram using NAND gates.

### Latch

Latches are digital circuits that stores a single bit of information and hold its values until it is updated by new input signals.

	Y2	Y1	X1	X0		
Z1	00	01	11	10	0	0000
Z0	1	1			1	

8421  
7010

$$F = \bar{X}\bar{Y}\bar{Z} + \bar{W}\bar{Y}\bar{Z} + \bar{W}\bar{X}Z + WY\bar{Z}$$

(ii)  $D(W, X, Y, Z) = \Sigma(2, 5, 7, 15)$

	Y2	Y1	X1	X0	
Z1	00	01	11	10	0
Z0	1	1			1


$D = \bar{W}\bar{X}\bar{Y}\bar{Z} + \bar{W}\bar{X}Z + XYZ$

$\Rightarrow$  iv) Simplify the following Boolean function to minimize the number of literals.

$$F(W, X, Y, Z) = \Sigma(0, 1, 2, 3, 4, 5, 6, 12)$$

SR (Set-Reset) Latches are the simplest form of latches and are implemented using two inputs. The S input sets the output to 1 while the R input sets the output 0.

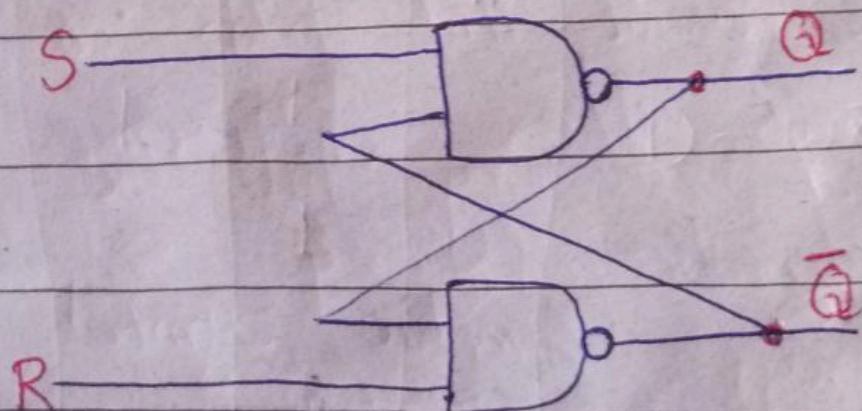When both are at 1 the latch said to be undefined.



What is the difference b/w  
Combinational & Sequential  
Circuits

Combinational Circuit      Sequential Circuit

- |   |  |
|---|--|
| * The output is dependent by on the current Input | * This output is dependent on both current & Previous output |
| * The Process is quick                            | * The Process is slow  |
| * It is simple                                    | * It is difficult to use & handle                            |

M T W T F S

5.5

\* Combinational circuits      \* Sequential circuits  
are incapable of      can store any  
storing any state      state or retain  
Previous states.

What is 4-bit binary Parallel  
Adder?

what is carry propagation time?

The carry Propagation Time is equal to the carry

M T W T F S


3.5

Propagation delay. The time required for a signal or waves to travel from one point of a transmission medium to another

What is T flip flop? Define Graphics symbol, characteristic table & equation.

T flip flop is a single input logic circuit that holds or toggles its output according to the input state.

(Graphic Symbol)

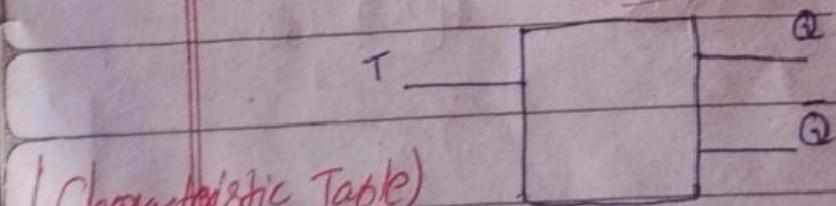

(Characteristic Table)

T	Q(t)	(Q(t+1))
---	------	----------

0	0	0
---	---	---

0	1	1
---	---	---

1	0	1
---	---	---

1	1	0
---	---	---

? Equation

$$Q(t+1) = \bar{T}(Q(t)) + T(\bar{Q}(t))$$

# 2020

(i) State the De Morgan's Theorem?

$$(i) (x+y)' = \bar{x} \cdot \bar{y}$$


$$(ii) (xy)' = \bar{x} + \bar{y}$$

(iii) what are the basic logic gates?


There are three basic logic gates

gates

• AND

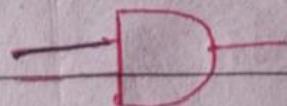

• OR

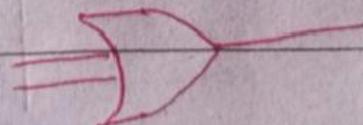

M T W T F S

not  $\rightarrow$

(iii) Convert Decimal to binary  
471

$$(100111001)_2$$

$$(111010111)_2$$

$$\begin{array}{r} 471 \\ \hline 2 | 235 \quad 1 \\ 2 | 117 \quad 1 \\ 2 | 58 \quad 1 \\ 2 | 29 \quad 0 \\ 2 | 14 \quad 1 \\ 2 | 7 \quad 0 \\ 2 | 3 \quad - \\ 1 \quad - \end{array}$$

(iv) Convert Decimal to octal  
103

$$(147)_8$$

$$\begin{array}{r} 103 \\ \hline 8 | 12 \quad 7 \\ 8 | 1 \quad - \\ 1 \quad - \end{array}$$

(v) Take 1's Complement of 546700  
decimal number

(Basically This is  
a wrong ①)

546700

(-15)

AB98F0

because not mention

which the given  
Question ~~belong~~  
belong

AB98F0 ↘

to which base)

Take 9's Compliment of 7291161  
binary number.

7291161

01110010100100101100001  
9's compliment  
10001101011011010011110

8421

Convert  $(F00EC2)_h$  to binary number

$(1110000000111011000010)_2$

write the truth table for

$$F = x + \bar{x} \cdot y + y$$


x	y	$x \cdot y$	$\bar{x} \cdot y$	$x + \bar{x} \cdot y + y$
0	0	0	0	0
0	1	0	1	1
1	0	0	1	1
1	1	1	1	1

Complement of the function  
 $F = x \cdot y + y \cdot x$ ?

$$(F)' = (x \cdot y + y \cdot x)'$$

$$\begin{aligned} F' &= (x \cdot y)' \cdot (y \cdot x)' \\ F' &= (\bar{x} + \bar{y}) \cdot (\bar{y} + \bar{x}) \end{aligned}$$

Graphical Symbol for AND Gate

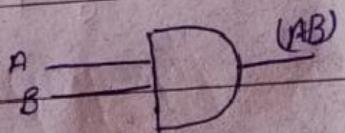

Registers in CPU:-

A register is a <sup>memory</sup> device in digital electronics that can store a specific amount of data bits. It is a group of flip-flops connected in series used to store multiple bits of data. The information stored within these registers can be transferred with the help of shift registers.

# Reduce A.B.A

$$A.B.A = A \cdot B$$

## Application of Flip-flop

Flip-flop application are <sup>use</sup> for

\* Temporary data storage as  
frequency dividers, and in counters

Data storage application a

group of flip flops are connected  
to parallel data lines and

clocked together. Data is stored  
until the next clock pulse.

## Define even Parity

Parity bit is an optional parameter, used in serial communication to determine if the data character being transmitted is correctly received by the remote device.

Parity bit may be even or odd even parity when we add zero as a extra parameter then this is called even parity.

## 2017

(iii) Express -99 as an 8 bit number in the Sign magnitude 2's Complement form.

Sign bit = -99

1	1	0	0	1	1	1	0	1
---	---	---	---	---	---	---	---	---

$\begin{array}{r} \text{Scomp} \\ \hline 0 & 0 & 1 & 1 & 1 & 0 & 0 \\ \text{dScomp} & & +1 \\ \hline 0 & 0 & 1 & 1 & 1 & 0 & 1 \end{array}$

2	9	9	
2	4	9	-1
2	2	4	-1
2	1	2	0
2	0	1	0
2	6	-0	
2	3	3	-6
2	1	1	-1

1100011

M T W T F S

Add the following binary

$$10110110 + 10011101$$

$$\begin{array}{r} 1 \overset{1}{0} \overset{1}{1} \overset{1}{0} 110 \\ + 10011101 \\ \hline 101010011 \end{array}$$

Simplify using Boolean Algebra techniques

$$A \cdot B + A \cdot (B+C) + B \cdot (B+C)$$

$$A \cdot B + A \cdot B + A \cdot C + B \cdot B + B \cdot C$$

According to distributive law

$$A \cdot B + A \cdot C + 0 + B \cdot C$$


$$A \cdot B + A \cdot C + BC$$

M T W T F S

State the De Morgan's Law to verify that NOR gate is used equivalent to NAND gate.

$$(x+y)' = \bar{x} \cdot \bar{y} \quad || \quad (xy)' = \bar{x} + \bar{y}$$

= 50

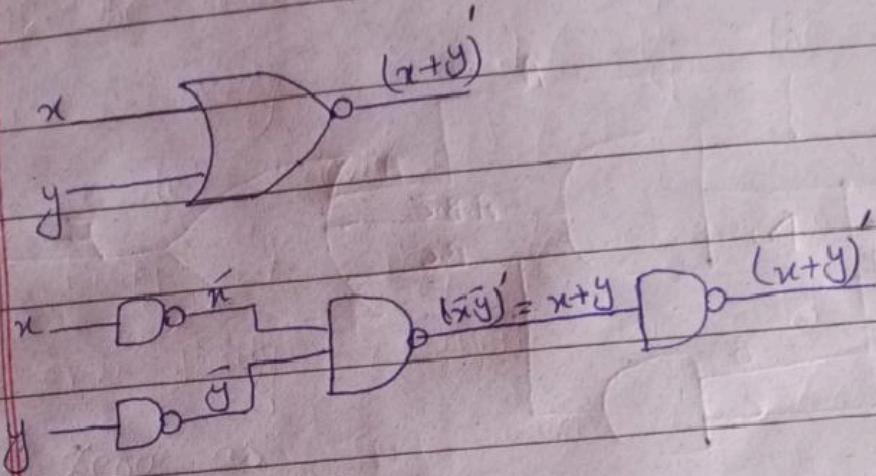


Prove that  $A + \bar{A} \cdot B = A + B$

A	B	$\bar{A}$	$\bar{A} \cdot B$	$A + \bar{A} \cdot B$	$A + B$
0	0	1	0	0	0
0	1	1	1	1	1
1	0	0	0	1	1
1	1	0	0	1	1

So prove Both are equal

Draw the gate Implementation of  
the function
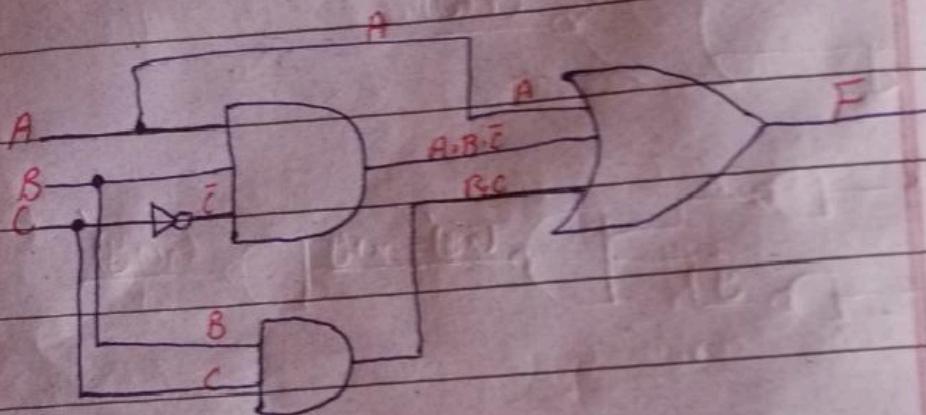
$$F = A + B \cdot C + A \cdot B \cdot \bar{C}$$



Minimize the following SOP using  
K-Map

$$F = A \cdot B \cdot C + \bar{A} \cdot B \cdot \bar{C} + \bar{A} \cdot \bar{B} \cdot \bar{C} + A \cdot \bar{B} \cdot C + A \cdot B \cdot \bar{C}$$

	BC	00	01	11	10
A	0	1			1
C	1		1	1	1

$$F = AC + \bar{A}\bar{C} + BC$$

M T W T F S


$$F = (A \oplus C) + BC$$

Determine the logic required to  
decode (1011)<sub>2</sub> by producing a High / HIGH  
on the output

$$\begin{aligned} &= 2^3 \times 1 + 2^2 \times 0 + 2^1 \times 1 + 2^0 \times 1 \\ &= 8 + 0 + 2 + 1 \end{aligned}$$


31

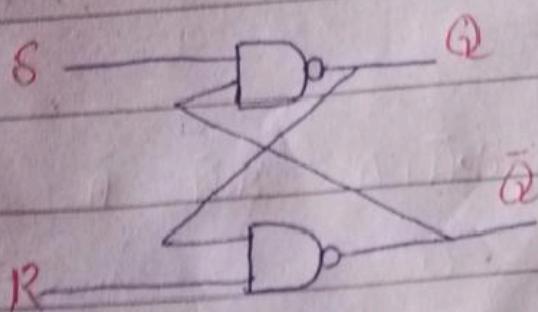Draw the diagram of SR-latch  
using NAND gate.



Difference b/w

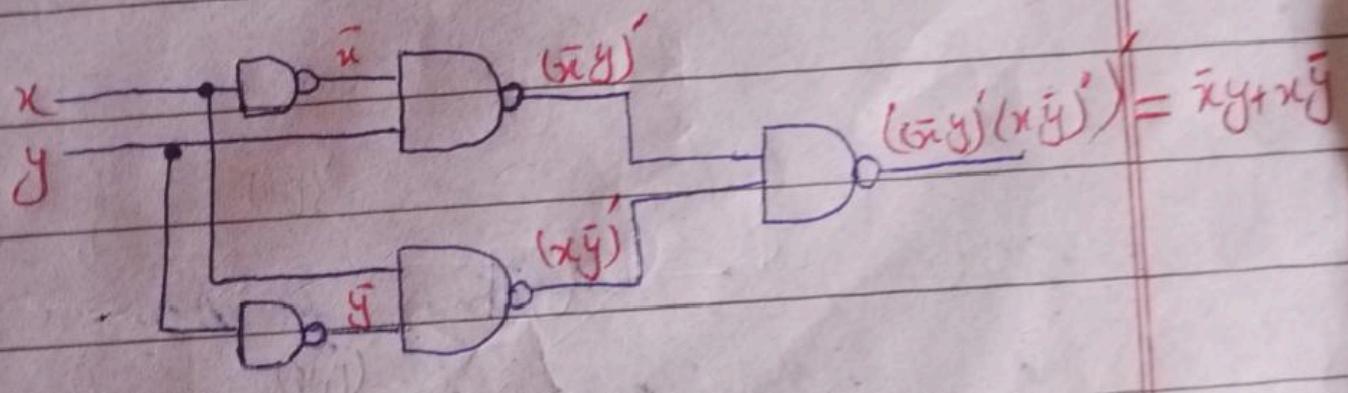Draw the logic diagram  
of an XOR gate using all  
NAND-gates.



2019

Use 10's Complement to Perform  
M-N when

$$M = 85320$$

$$M = 85320$$

$$N = \underline{8640}$$

$$\textcircled{1} 3960$$

$$M-N = 33960$$

$$N = 51360$$

a's complement

$$N^2 = \underline{48639}$$

10's complement

$$N = 138640$$

$$85320$$

$$51360$$

$$\textcircled{1} 3960$$

Write the following function  
into Minterms

$$F_1 \Sigma (2,4,5,6)$$

$$F_2 \Pi (0,1,3,7)$$

M T W T F S

Using Postulates & Theorems  
of Boolean algebra Prove  
 $x + xy = x$


$$x(1+y) = x$$

$$x(1) = x$$

$$x = x$$


Simplify using K-Map

$$F(A,B) = A'B' + AB' + AB$$

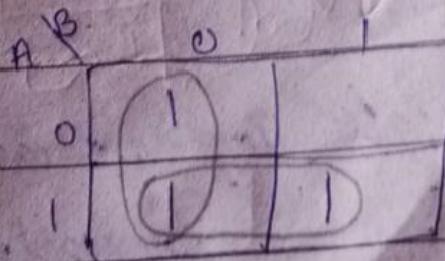

$$F_2 = \bar{B} + A$$

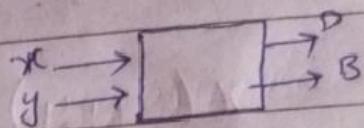Draw the truth table of half subtractor  
and write the Boolean function for  
its Borrow and Difference?




x	y	D	B
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

What is Karnaugh?

K-Map  
↓  
Karnaugh

Draw the gate Implementation  
of the following expression

$$F = AB + A(B+C) + B(B+C)$$

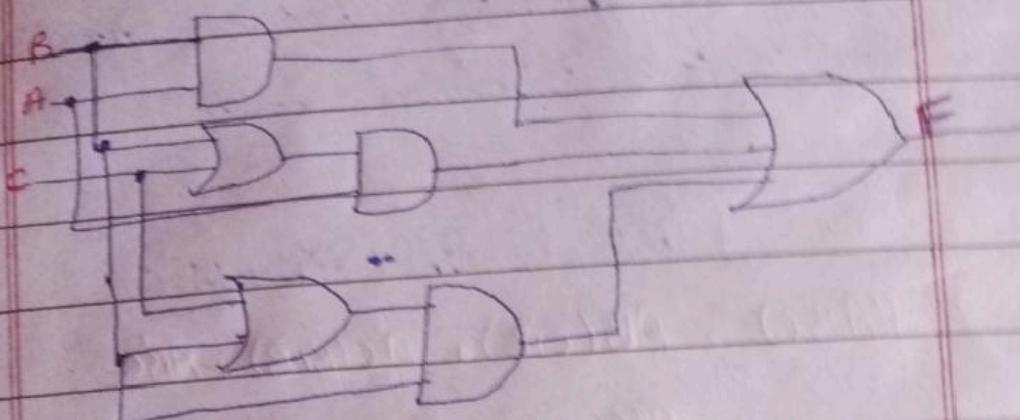

Prove that exclusive-OR is the  
Complement of exclusive-NOR!

$$(x \oplus y) = (\bar{x}y + x\bar{y})$$

Take complement on b.c

$$\begin{aligned}(x \oplus y)' &= (\bar{x}y + x\bar{y})' \\ &= (\bar{x}y)' \cdot (x\bar{y})' \\ &= (x + \bar{y})(\bar{x} + y)\end{aligned}$$

$$\begin{aligned}&= x\bar{x} + xy + \bar{x}\bar{y} + y\bar{y} \\ &= 0 + xy + \bar{x}\bar{y} + 0 \\ &= xy + \bar{x}\bar{y}\end{aligned}$$

$$(x \oplus y)' = x \odot y$$

∴ Prove.

M T W T F S

Ex

Expand the following Boolean functions  
into their canonical form

$$f(A, B, C) = AB + A'C + AB'C$$

$$f(A, B, C) \rightarrow AB(C + \bar{C}) + A'C(B + \bar{B}) + AB\bar{C}$$

$$\rightarrow ABC + ABC + A'BC + A'B'C + AB'C$$

What is 4-bit binary Parallel  
adder?

## Minterm:

Minterms are the Product of all the variables in a Boolean function where each variable appears exactly once in true or complement form

## Maxterm:

Maxterm are sum of all the variables in a Boolean function where each variable appears exactly once in true or complement form

## Don't Care Condition:

The case Some conditions whose output cannot be specified so we use don't care conditions in that case. To make a group of cells we also ignore that cells. We mainly use "don't care" cell to make a large group of cells.

How many types of number  
System are there?

Four  
The four most common  
number system types are these:

Decimal No System (Base 10)

Binary No System (Base 2)

Octal No System (Base 8)

Hexadecimal No System (Base 16)

## Duality Principle:

This Principle states  
that

\* Changing every OR into AND and  
vice versa.

\* Changing every 0 into 1 and  
vice versa.

## Parity bit:

Parity bit is an optional parameter, used in serial communication to determine if the data characters being transmitted is correctly received by the remote device.

Parity bit may be placed on left side or right side

Parity bit may be odd or even.

## K-Map:

K-Map is a visual method used to simplify the algebraic expressions in Boolean functions without having to resort to complex theorems or equation manipulations.

## End carry:

The carry out of last digit is called end carry.

**Catty:**

To take something or  
someone to a particular point or  
in a particular direction.

## Multiplexers:

It is a combinational circuit which have many data inputs and single output depending on Control or Select Inputs.

### Example:

In telephone network multiple audio signals are integrated on a single line for transmission with the help of multiplexers.

## Demultiplexers:

A demultiplexer. Sometimes abbreviated dmenu, is a circuit that has one input and more than one output. It is used when a circuit intends

to send a signal to one of many devices

## De-Codes:-

A combinational logic circuit which has  $n$  input lines and minimum  $2^n$  output lines is known as decoder. Decoder is an electronic device that converts signals from one form to another.

## Encoder:-

An encoder is a sensing device that provides feedback. Encoder converts motion to an electrical signal that can be read by some type of control device in a motion control system.

## Clock Pulse:-

The clock

M T W T F S

8.5

Pulses are at a frequency that is much higher than the sampling pulses, and while a voltage is being held at the input, the clock pulses pass through the gate and are counted.