

Chapter - 7

①

$$\begin{array}{ll} N_1 = 100 & N_2 = 600 \\ V_1 = 120V & V_2 = ? \\ I_1 = 12A & I_2 = ? \end{array}$$

$$K = \frac{N_2}{N_1} = \frac{600}{100} = 6$$

$$V_2 = KV_1$$

$$V_2 = 6 \times 120$$

$$= 720V$$

$$I_2 = \frac{I_1}{K} = \frac{12}{6}$$

$$I_2 = 2A$$

②

$$\begin{array}{lll} V_1 = 240V & V_2 = 12V & \\ I_1 = ? & K = ? & I_2 = 40A \end{array}$$

$$V_2 = KV_1$$

$$K = \frac{V_2}{V_1}$$

$$K = \frac{12}{240} = \frac{1}{20}$$

$$\frac{N_2}{N_1} = \frac{1}{20}$$

$$I_2 = \frac{I_1}{K}$$

$$K = \frac{I_1}{I_2} \quad I_1 = KI_2$$

$$I_1 = \frac{1}{20} \times 40$$

$$I_1 = 2A$$

Q

K in term of impedance $= K = \sqrt{Z_2/Z_1}$

- P-N Junction - Diode

$$\begin{aligned} V_B &= ? \\ a &= 100^\circ\text{C} & b &= 0^\circ\text{C} \\ t &= 25^\circ\text{C} & & 0.7\text{V} \end{aligned}$$

(a).

$$\begin{aligned} \Delta V_B &= -0.002 \Delta t \\ \Delta t &= t_2 - t_1 \\ \Delta t &= 100 - 25^\circ = 75^\circ \end{aligned}$$

$$\Delta V_B = -0.002 \times 75^\circ = -0.015\text{V}$$

$$\begin{aligned} V_B \text{ at } 100^\circ\text{C} &= 0.7 + (-0.015\text{V}) \\ &= 0.7 - 0.015\text{V} \\ &= 0.685\text{V} \end{aligned}$$

(b).

$$\begin{aligned} \Delta V_B &= -0.002 \Delta t \\ \Delta t &= 0^\circ - 25^\circ \\ \Delta t &= -25^\circ \end{aligned}$$


$$\begin{aligned} \Delta V_B &= -0.002 \times (-25^\circ) \\ &= 0.05\text{V} \end{aligned}$$

V_B at 25°C

$$\begin{aligned} V_B &= 0.7 + 0.05 \\ &= 0.75\text{V} \end{aligned}$$

Req = 2
I = ?

branch current.

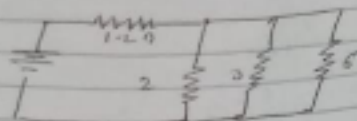

- Voltage drop across R_1

- $V_{R1} = 5 \times 0.2 = 1V$
Current through R_1 will be same because it is in series.

- Voltage across R_{234} will be same because they are in parallel which is 5V.

- Current through R_2

$$I_{R2} = V/R \Rightarrow 5/2 = 2.5A$$


- Current through R_3

$$I_{R3} = V/R \Rightarrow 5/3 = 1.66A \\ = 1.7A$$

- Current through R_4


$$I_{R4} = V/R \Rightarrow 5/6 \Rightarrow 0.83A \\ 0.8A$$

1)

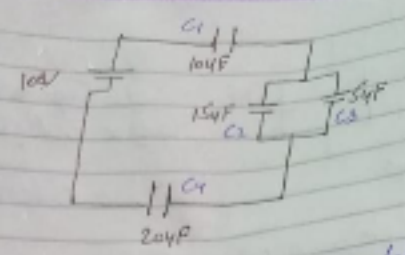

$C_{eq} = ?$
 $Q = ?$

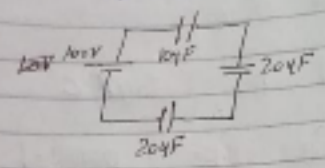C_2 and C_3 are parallel so,
 $C_{23} = C_2 + C_3$
 $= 15 + 5 \Rightarrow 20\mu F$



No all are in series so,

$$\frac{1}{C_{eq}} = \frac{1}{10} + \frac{1}{20} + \frac{1}{20}$$


$$\frac{2+1+1}{20} = \frac{4}{20}$$

$$C_{eq} = 20/4 = 5\mu F$$

- Now Lets find charge through each capacitor but we have to find voltage drop across each capacitor.
- Voltage is same for parallel but it is divided in series. as ~~current~~ charge is alternative of it.

Total Charge:
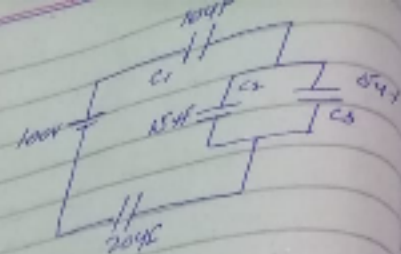
$$\begin{aligned} Q &= CV \\ Q_0 &= C_0 V \\ &= 5 \times 100 \\ &= 500 \mu C \end{aligned}$$



Let calculate charge through each capacitor.

Charge through C_1 will be same because it is connected in series. that is $500 \mu C$.

Charge through C_2 and C_3 will be obtained by formula,

$$\begin{aligned} Q_2 &= Q_0 \left(\frac{C_2}{C_2 + C_3} \right) \\ &= 500 \left(\frac{15}{20} \right) = 375 \mu C \end{aligned}$$

$$Q_3 = Q_0 \left(\frac{C_3}{C_2 + C_3} \right)$$

$$Q_3 = 500 \left(\frac{5}{20} \right) = 125 \mu C$$


Charge through C_4 will $500 \mu C$ as it is in series.

Voltage through each capacitor.
Voltage drop across C_1

$$Q = CV$$

$$V = Q/C$$
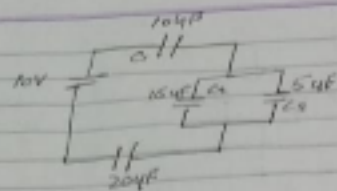
$$\Rightarrow \frac{500}{10} \Rightarrow 50 \text{ volts}$$



$$Q = CV$$

$$Q = 5\mu F \times 10$$

$$Q = 50\mu C$$

$$\therefore C \text{ (coulomb)}$$

Voltage drop across C_1

$$Q = CV, \quad V = Q/C$$

$$V_1 = \frac{50}{10} = 5 \text{ volts}$$

Current will be $50\mu C$

C_2 and C_3 are parallel to each other so voltage will be same which is 5 volts. Charge (Q) will be divided.

Charge through C_2

$$Q_{C2} = \frac{C_2}{C_2 + C_3} \times Q = \frac{15}{5} = 30\mu C$$

Charge through C_3

$$Q_{C3} = \frac{C_3}{C_2 + C_3} \times Q = \frac{5}{5} = 10\mu C$$

$$Q_{C2} = Q_1 \left(\frac{C_2}{C_2 + C_3} \right)$$


$$= 50 \left(\frac{15}{20} \right) \Rightarrow 37.5\mu C$$

$$= 50 \left(\frac{5}{20} \right) \Rightarrow \underline{\underline{12.5}}$$

Paper - 2018
Numericals

$R_{eq} = ?$
 $I = ?$


1)

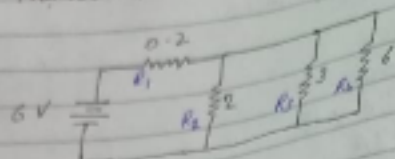

R_2, R_3, R_4 are in parallel so,


$$\frac{1}{R_{eq}} = \frac{1}{2} + \frac{1}{3} + \frac{1}{6}$$
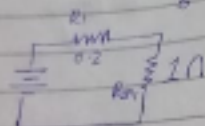
$$\frac{1}{R_{eq}} = \frac{3+2+1}{6} = \frac{6}{6} = 1 \Omega$$



$$R_{eq} = 0.2 + 1$$

$$= 1.2 \Omega$$

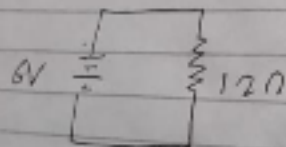

Current $I = \frac{V}{R} \Rightarrow \frac{6}{1.2} = 5A$

Power $P = VI \Rightarrow 6 \times 5 = 30 \text{ watt}$
 $= I^2 R \Rightarrow 5^2 \cdot 1.2 = 30 \text{ watt}$

- If short circuit happens infinite current will flow through the circuit.