University of Sargodha

BS 1st Term Examination 2023

Paper: Applied Physics/Basic Electronics (PHYS-101/PHY-2210) Subject: CS/IT

Time Allowed: 02:30 Hours Maximum Marks: 60

Note: Objective part is compulsory. Attempt any four questions from subjective part.

(Compulsory) Objective Part


0.1. Write short answers of the following in 2-3 lines each on your answer sheet.

(2*12)

- · i. What is analog modulation and state various techniques?
- ji. Give the advantages of PIN photodiodes.
- How the op-amp comparator should be chosen to get higher speed of operation?
- In an NPN silicon transistor, α=0.995, I_E=10mA and leakage current I_{CBO}=0.5μA. Determine I_{CBO}
- What does ICEO, the subscript 'CEO' means?
- vi. In a BJT, the collector current is 12 mA and the emitter current is 1.02 times the collector current. Find the base current.
- VI. Define the different operating regions of transistor.
- · viii. . What is meant by diffusion capacitance?
- Derive the ripple factor of full wave rectifier.
- . · X. What is meant by drift current?
- . . xi. Define magnetic reluctance.
 - Two capacitors of capacitance $C_1 = 6 \mu$ F and $C_2 = 3 \mu$ F are connected in series across a cell of emf 18 V. Calculate the charge on each capacitor.

(4*9)Subjective Part

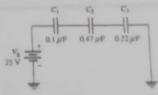- a) What is difference between active and passive components? Give some examples of these components. O.2.
 - b) State three quantities which are used to establish Ohm's law for magnetic circuits,
 - c) Find the voltage across each capacitor.



- - a) What is meant by isolated atom, draw the energy levels of an isolated atom.
 - b) Differentiate solid by using energy band diagram.
 - c) A silicon diode has a forward voltage drop of 1.2 V for a forward dc current of 100 mA. It has a reverse current of 1µA for the reverse voltage of 10 V. calculate. Bulk and reverse resistance of the diode.
- a) What are different types of power supply. Draw block diagram of dc power supply. 0.4.
 - b) What is rectifier? Discuss the working of center tapped transformer full wave rectifier and calculate its average value.
 - c) For a silicon diode, the reverse saturation current at room temperature (T = 300 K) is found to be 100 nA. What should be diode current when the applied voltage is (a) 0.2 V (b) 0.8 V?
- a) What is voltage multiplier? Discuss the working of half-wave voltage doubler. Q.5.
 - b) Draw transistor circuit configuration and determine the relation between α and β .
 - c) An AC supply of 230 V is applied to a half-wave rectifier circuit through a transformer of turn ratio 10:1. Find (i) the output d.c. voltage and (ii) the peak inverse voltage. Assume the diode to be ideal.
 - a) What is meant by leakage current in a transistor? How these can be classified.
- Show that $I_C = \beta I_B + (\beta + 1)I_{CBO}$.
 - b) What is difference between intrinsic and extrinsic semiconductor? How extrinsic semiconductors are fabricated.
 - c) What is difference between real and ideal diode?
- a) What is difference between Modulation and De-modulation? State different types of modulation. b) An audio signal given by 15sin2π(2000)t amplitude-modulates a sinusoidal sine wave 60sin2π(100,000) Q.7.
 - determine modulation index, percent modulation, frequencies of signal and carrier, channel width,
 - c) What is solar cell? Discuss the working of solar cell.